

Digital Design & Computer Arch.

Lecture 5: Combinational Logic II

Prof. Onur Mutlu

ETH Zürich

Spring 2021

11 March 2021

Assignment: Required Lecture Video

- Why study computer architecture? Why is it important?
- Future Computing Platforms: Challenges & Opportunities
- **Required Assignment**
 - ❑ **Watch one of** Prof. Mutlu's lectures and analyze either (or both)
 - ❑ <https://www.youtube.com/watch?v=kgiZISOcGFM> (May 2017)
 - ❑ <https://www.youtube.com/watch?v=mskTeNnf-i0> (Feb 2021)
- **Optional Assignment – for 1% extra credit**
 - ❑ **Write a 1-page summary** of one of the lectures and email us
 - What are your key takeaways?
 - What did you learn?
 - What did you like or dislike?
 - Submit your summary to [Moodle](#) – Deadline: April 5

Assignment: Required Readings

■ This week

□ Combinational Logic

- P&P Chapter 3 until 3.3 + H&H Chapter 2

■ Next week

□ Hardware Description Languages and Verilog

- H&H Chapter 4 until 4.3 and 4.5

□ Sequential Logic

- P&P Chapter 3.4 until end + H&H Chapter 3 in full

■ By the end of next week, make sure you are done with

- **P&P Chapters 1-3 + H&H Chapters 1-4**


Modern General-Purpose Microprocessors

5-nanometer process


The first personal computer chip built with this cutting-edge technology.

16 billion transistors

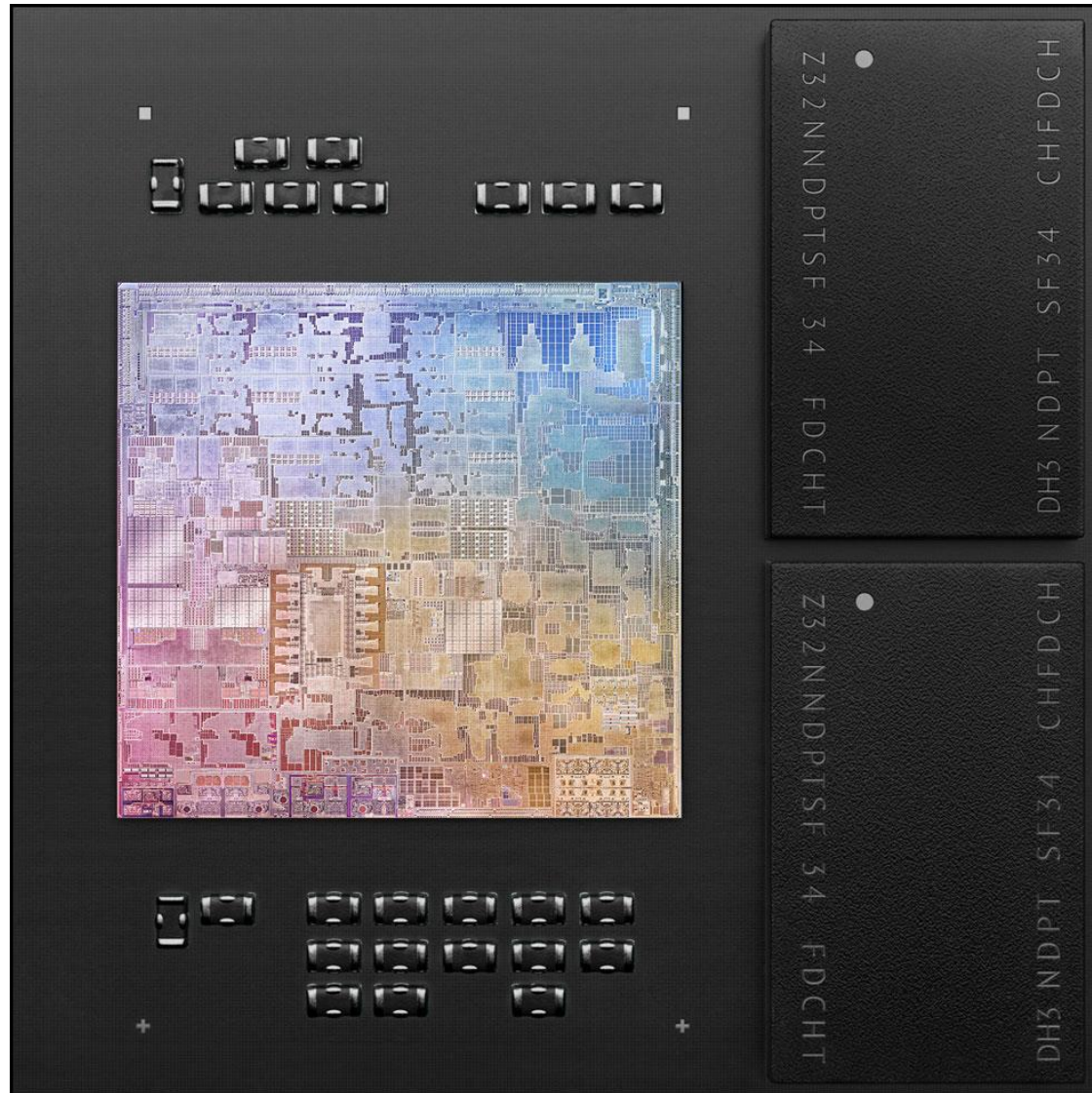The most we've ever put into a single chip.




Modern General-Purpose Microprocessors

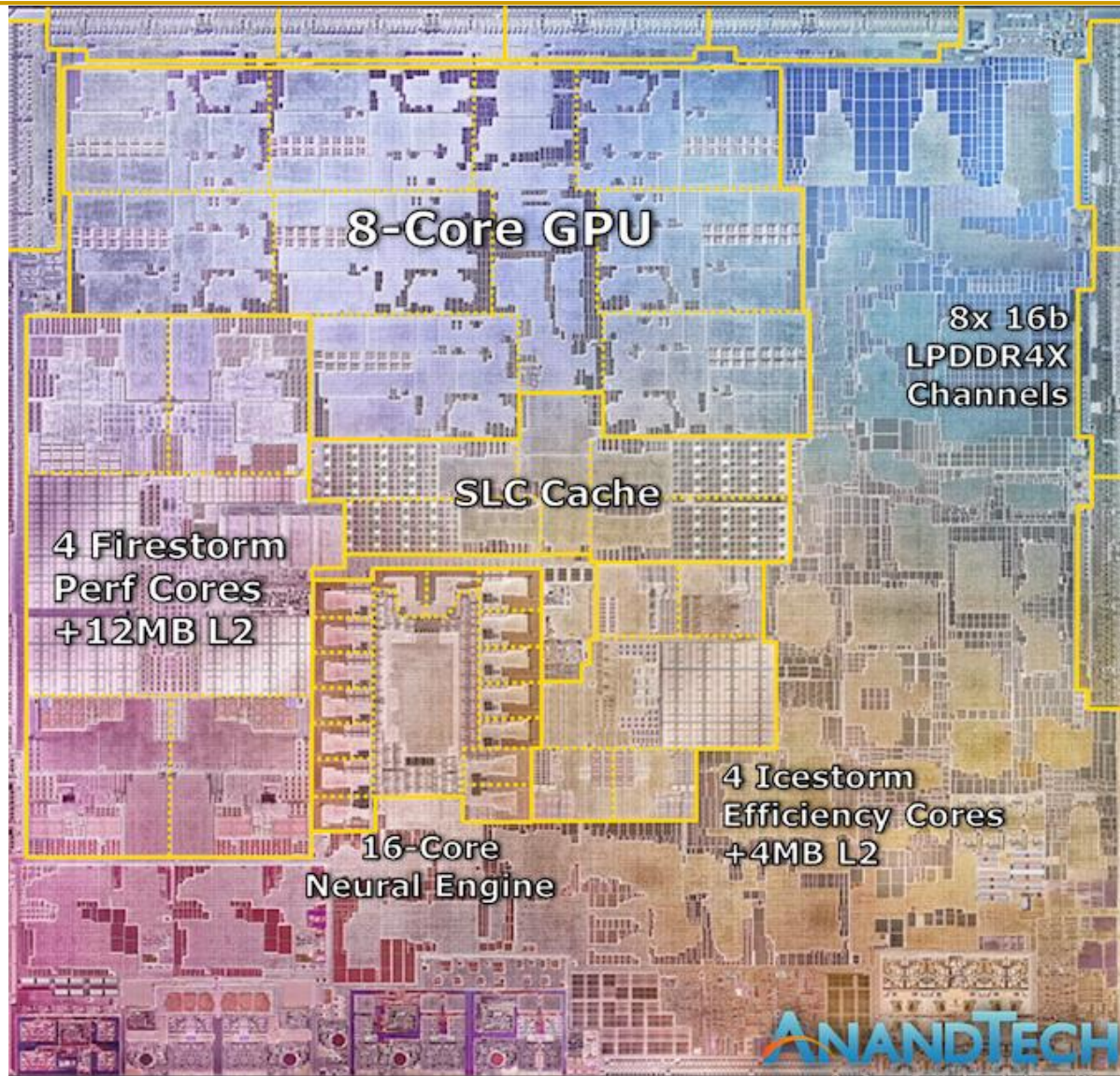


FPGAs



Modern FPGAs

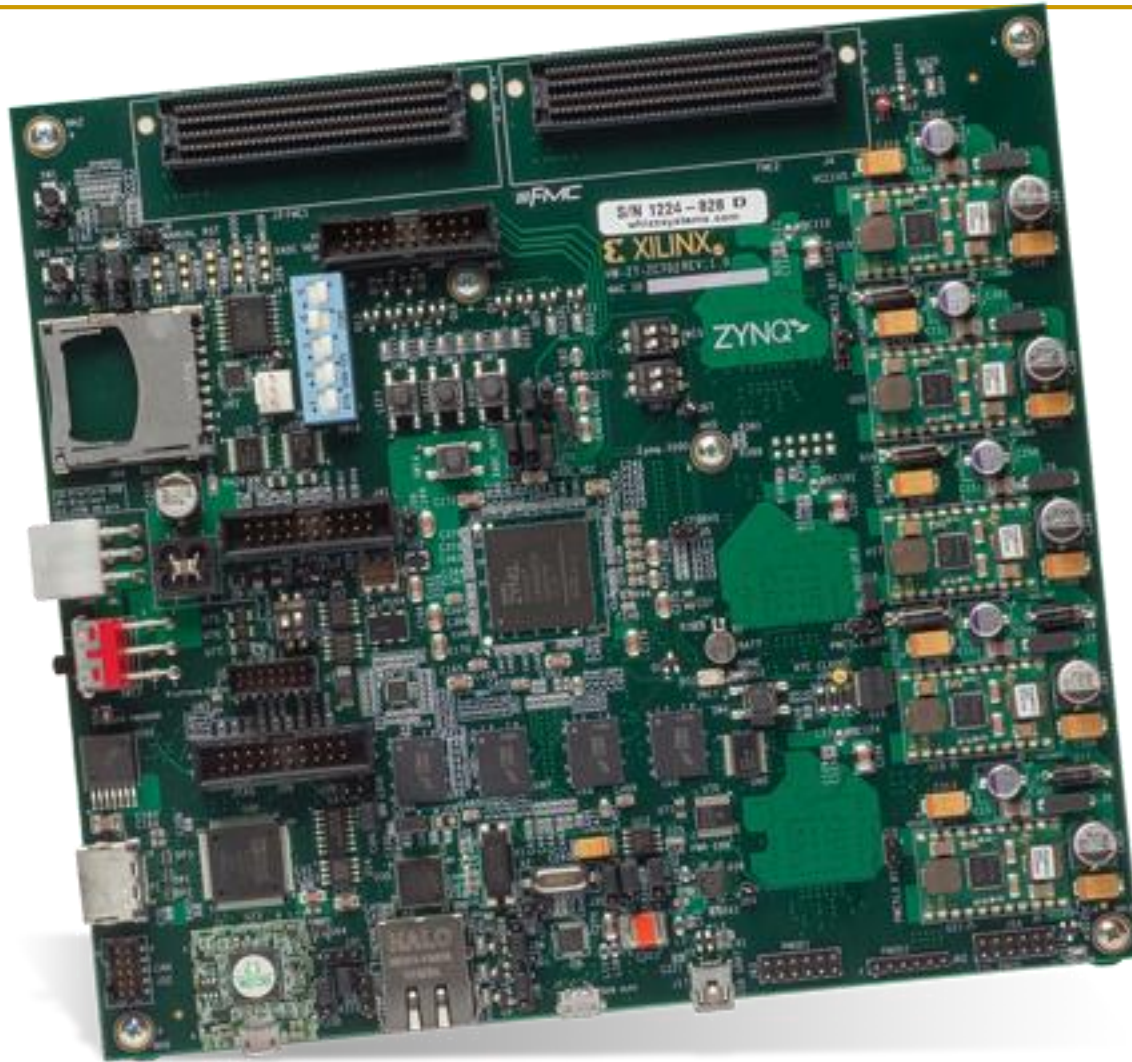

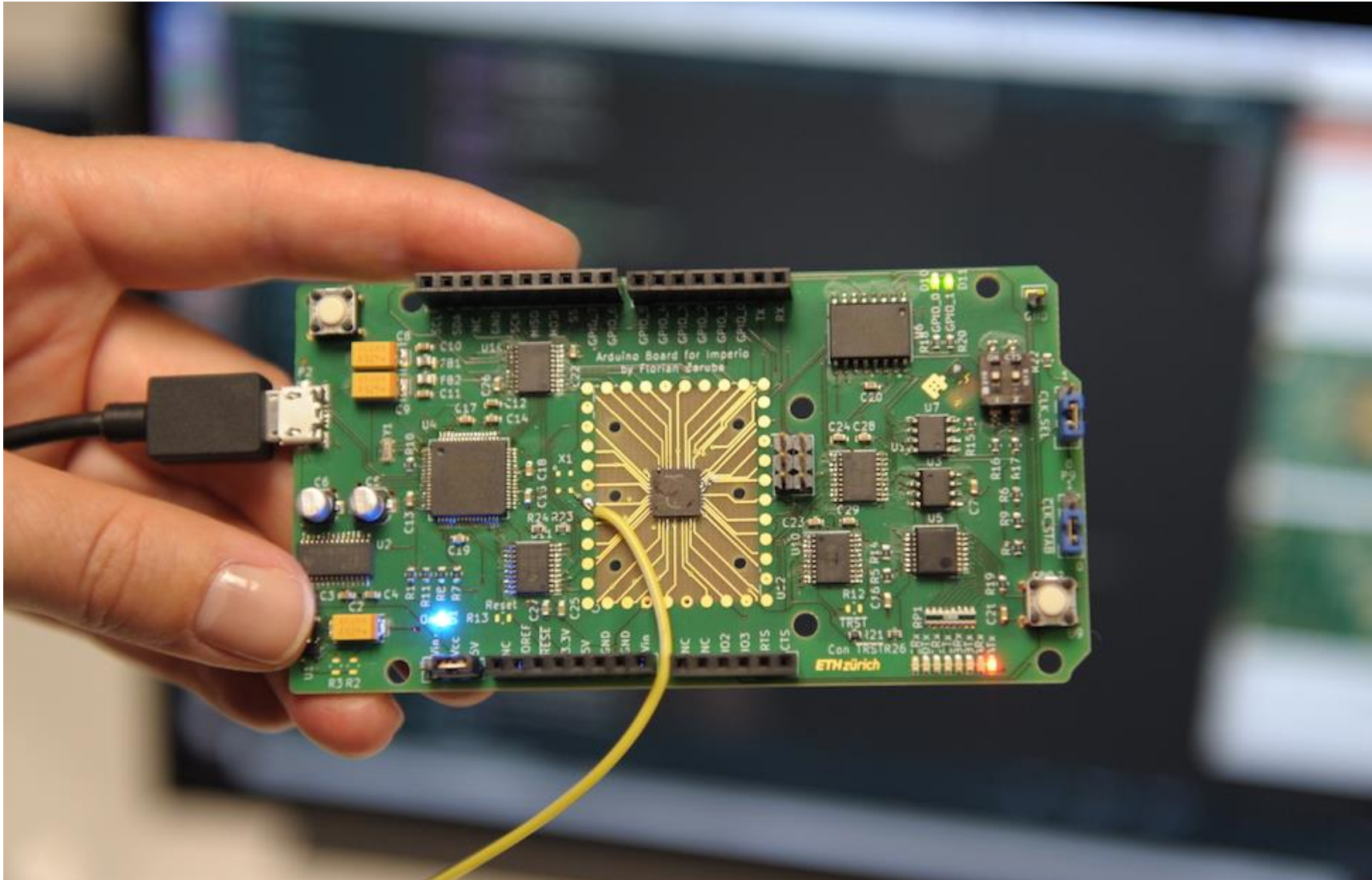Special-Purpose ASICs (App-Specific Integrated Circuits)



Modern Special-Purpose ASICs

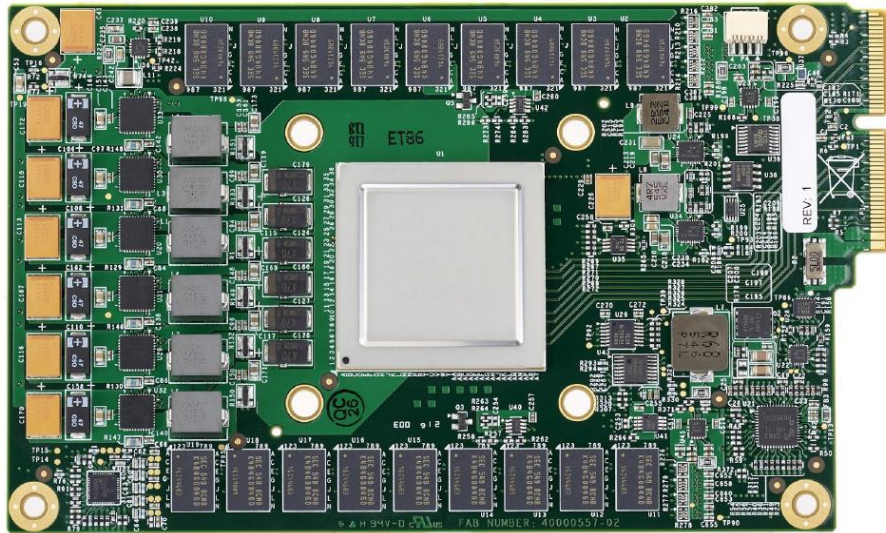


Figure 3. TPU Printed Circuit Board. It can be inserted in the slot for an SATA disk in a server, but the card uses PCIe Gen3 x16.


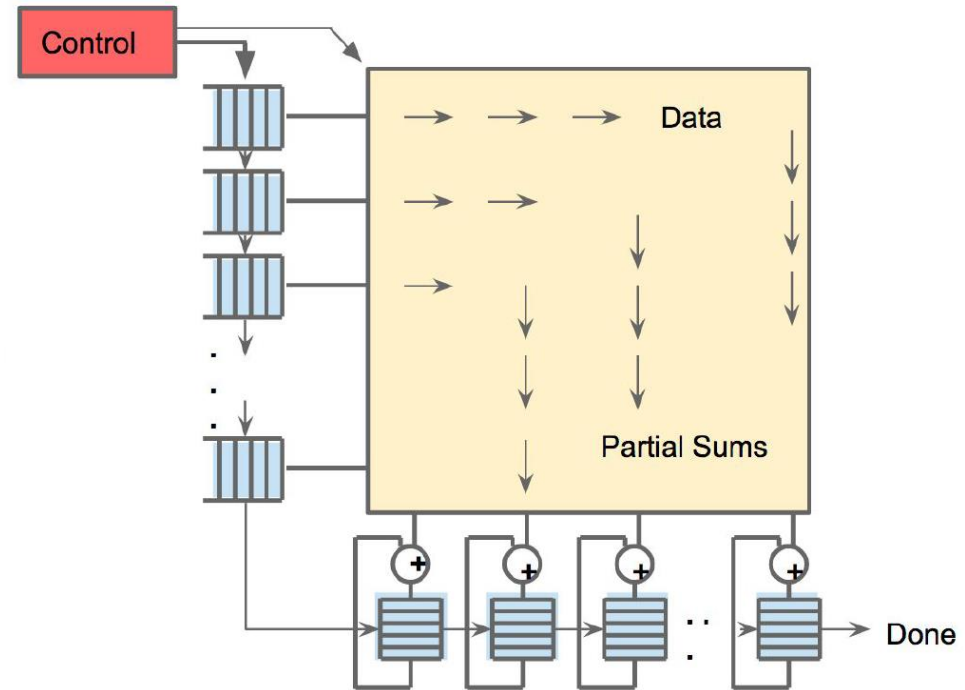


Figure 4. Systolic data flow of the Matrix Multiply Unit. Software has the illusion that each 256B input is read at once, and they instantly update one location of each of 256 accumulator RAMs.

Jouppi et al., “In-Datcenter Performance Analysis of a Tensor Processing Unit”, ISCA 2017.

Modern Special-Purpose ASICs

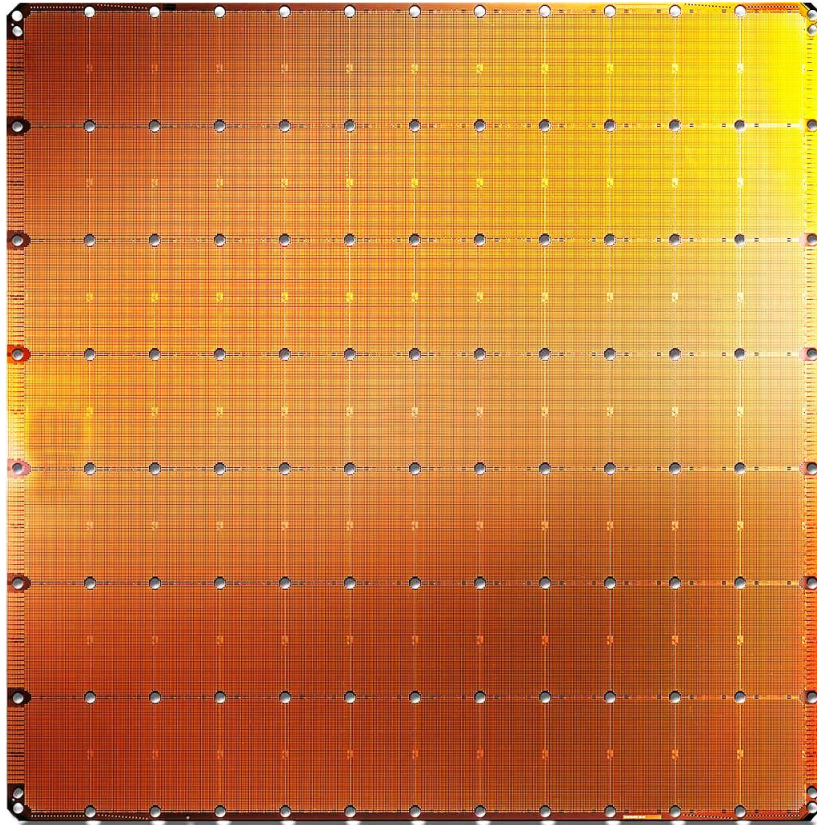

Cerebras WSE

1.2 Trillion transistors
46,225 mm²

- The largest ML accelerator chip
- 400,000 cores



Largest GPU


21.1 Billion transistors
815 mm²

NVIDIA TITAN V

<https://www.anandtech.com/show/14758/hot-chips-31-live-blogs-cerebras-wafer-scale-deep-learning>

<https://www.cerebras.net/cerebras-wafer-scale-engine-why-we-need-big-chips-for-deep-learning/> 10

Modern GPUs

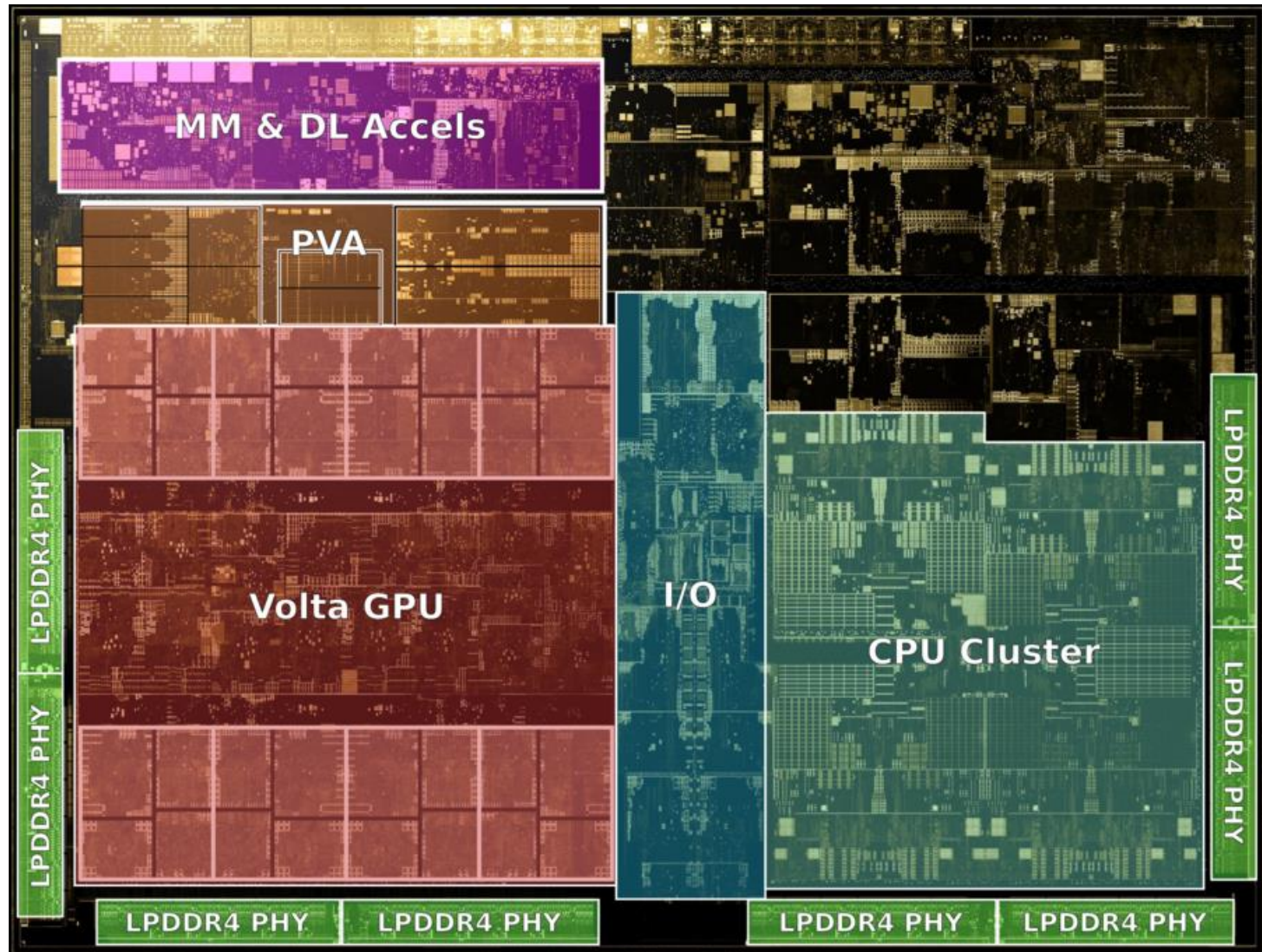


Combinational Logic Circuits and Design

What We Will Learn in This Lecture


- Building blocks of modern computers
 - Transistors
 - Logic gates
- Combinational circuits
- Boolean algebra
- How to use Boolean algebra to represent combinational circuits
- Minimizing logic circuits

Recall: Transistors and Logic Gates

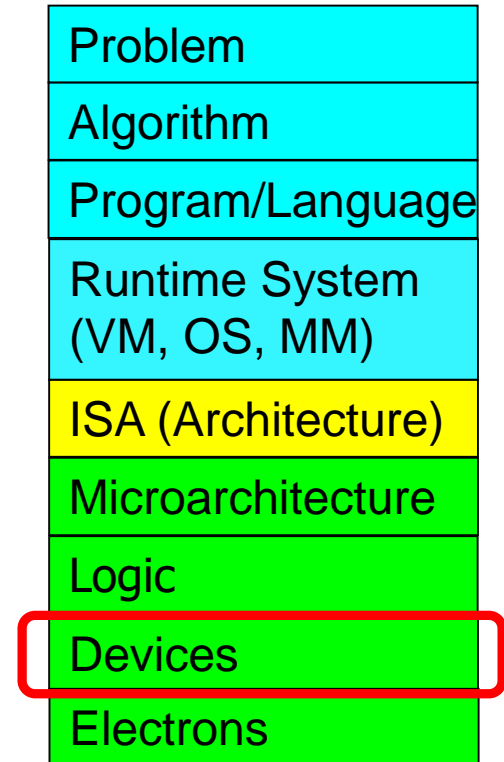
- **Now, we know how a MOS transistor works**
- How do we build logic out of MOS transistors?
- **We construct basic logic structures out of individual MOS transistors**
- These **logical units** are named **logic gates**
 - They implement simple **Boolean** functions




Recall: CMOS NOT, NAND, AND Gates

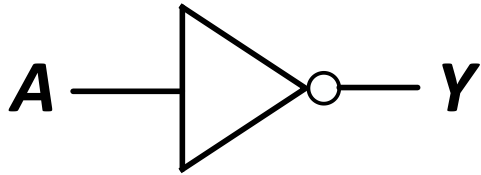




A	Y
0	1
1	0

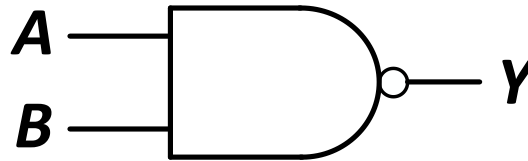

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

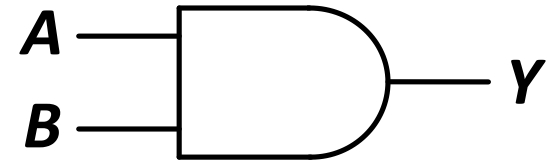

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

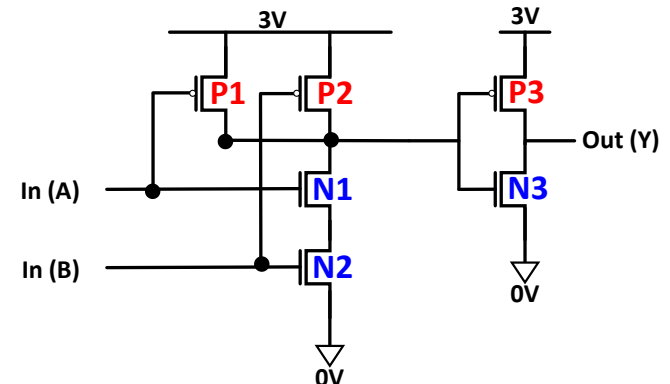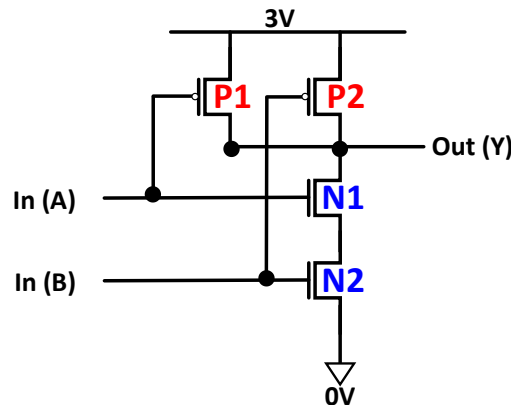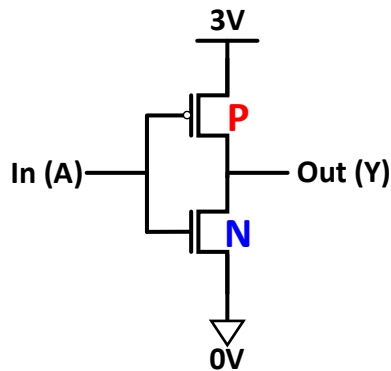

Recall: Common Logic Gates

Buffer



A	Z
0	0
1	1

AND



A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

XOR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

Inverter



A	Z
0	1
1	0

NAND



A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

NOR



A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

XNOR




A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

Boolean Equations

Recall: Functional Specification

- **Functional specification** of outputs in terms of inputs
- What do we mean by “function”?
 - Unique **mapping** from input values to output values
 - The **same** input values produce the **same** output value every time
 - **No memory** (does not depend on the history of input values)
- **Example (full 1-bit adder – more later):**

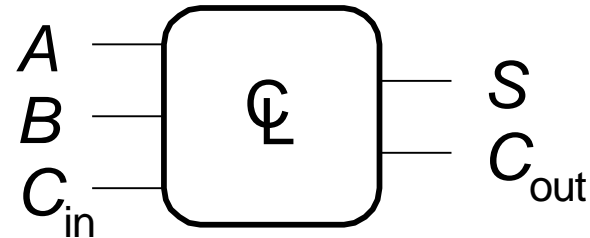
$$\begin{aligned} S &= F(A, B, C_{in}) \\ C_{out} &= G(A, B, C_{in}) \end{aligned}$$



$$\begin{aligned} S &= A \oplus B \oplus C_{in} \\ C_{out} &= AB + AC_{in} + BC_{in} \end{aligned}$$

Recall: Boolean NOT / AND / OR

\bar{A} (reads “not A”) is 1 iff A is 0

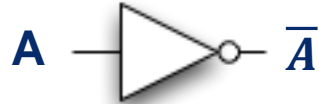

A	\bar{A}
0	1
1	0

$A \cdot B$ (reads “A and B”) is 1 iff A and B are both 1



A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

$A + B$ (reads “A or B”) is 1 iff either A or B is 1



A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Recall: Boolean Algebra: Axioms

Formal version

1. B contains at least two elements,
 0 and 1 , such that $0 \neq 1$

2. *Closure* $a, b \in B$,
(i) $a + b \in B$
(ii) $a \cdot b \in B$

3. *Commutative Laws*: $a, b \in B$,
(i)
(ii)

4. *Identities*: $0, 1 \in B$
(i)
(ii)

5. *Distributive Laws*:
(i)
(ii)

6. *Complement*:
(i) $\overline{\overline{a}} = a$
(ii) $a + \overline{a} = 1$
 $a \cdot \overline{a} = 0$

English version

Math formality...

Result of AND, OR stays
in set you start with

For primitive AND, OR of
2 inputs, order doesn't matter

There are identity elements
for AND, OR, that give you back
what you started with

- distributes over $+$, just like algebra
...but $+$ distributes over \cdot , also (!!)

There is a complement element;
AND/ORing with it gives the identity elm.

Recall: Boolean Algebra: Duality

■ Observation

- All the axioms come in “dual” form
- Anything true for an expression also true for its dual
- So any derivation you could make that is true, can be flipped into dual form, and it stays true

■ Duality — More formally

- A dual of a Boolean expression is derived by replacing
 - Every AND operation with... an OR operation
 - Every OR operation with... an AND
 - Every constant 1 with... a constant 0
 - Every constant 0 with... a constant 1
 - But don't change any of the literals or play with the complements!

Example

$$\begin{aligned} a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ \rightarrow a + (b \cdot c) &= (a + b) \cdot (a + c) \end{aligned}$$

Recall: Boolean Algebra: Useful Laws

Operations with 0 and 1:

1. $X + 0 = X$
2. $X + 1 = 1$

Dual
↓

1D. $X \cdot 1 = X$
2D. $X \cdot 0 = 0$

AND, OR with identities
gives you back the original
variable or the identity

Idempotent Law:

3. $X + X = X$

3D. $X \cdot X = X$

AND, OR with self = self

Involution Law:

4. $\overline{\overline{X}} = X$

double complement =
no complement

Laws of Complementarity:

5. $X + \overline{X} = 1$

5D. $X \cdot \overline{X} = 0$

AND, OR with complement
gives you an identity

Commutative Law:

6. $X + Y = Y + X$

6D. $X \cdot Y = Y \cdot X$

Just an axiom...

Recall: Useful Laws (continued)

Associative Laws:

$$\begin{aligned} 7. (X + Y) + Z &= X + (Y + Z) \\ &= X + Y + Z \end{aligned}$$

$$\begin{aligned} 7D. (X \cdot Y) \cdot Z &= X \cdot (Y \cdot Z) \\ &= X \cdot Y \cdot Z \end{aligned}$$

Parenthesis order
does not matter

Distributive Laws:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z) \quad \text{Axiom}$$

Simplification Theorems:

9.

9D.

10.

10D.

11.

11D.

Useful for
simplifying
expressions

Actually worth remembering — they show up a lot in real designs...

Boolean Algebra: Proving Things

Proving theorems via axioms of Boolean Algebra:

EX: Prove the theorem: $X \cdot Y + X \cdot \bar{Y} = X$

Distributive (5)

Complement (6)

Identity (4)

EX2: Prove the theorem: $X + X \cdot Y = X$

Identity (4)

Distributive (5)

Identity (2)

Identity (4)

DeMorgan's Law: Enabling Transformations

DeMorgan's Law:

$$12. \overline{(X + Y + Z + \dots)} = \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot \dots$$

$$12D. \overline{(X \cdot Y \cdot Z \cdot \dots)} = \bar{X} + \bar{Y} + \bar{Z} + \dots$$

■ Think of this as a transformation

- Let's say we have:

$$F = A + B + C$$

- Applying DeMorgan's Law (12), gives us

$$F = \overline{\overline{(A + B + C)}} = \overline{(\bar{A} \cdot \bar{B} \cdot \bar{C})}$$

At least one of A, B, C is TRUE --> It is **not** the case that A, B, C are **all** false

DeMorgan's Law (Continued)

These are conversions between **different types of logic functions**
They can prove useful if you do not have **every type of gate**

$$A = \overline{(X + Y)} = \bar{X}\bar{Y}$$

**NOR is equivalent to AND
with inputs complemented**



X	Y	$\overline{X + Y}$	\bar{X}	\bar{Y}	$\bar{X}\bar{Y}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0

$$B = \overline{(XY)} = \bar{X} + \bar{Y}$$

**NAND is equivalent to OR
with inputs complemented**



X	Y	\overline{XY}	\bar{X}	\bar{Y}	$\bar{X} + \bar{Y}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

Using Boolean Equations to Represent a Logic Circuit

Sum of Products Form: Key Idea

- Assume we have the truth table of a Boolean Function
- How do we express the function in terms of the inputs in a **standard** manner?
- Idea: **Sum of Products** form
- Express the truth table as a two-level Boolean expression
 - that contains **all** input variable combinations that result in a 1 output
 - If ANY of the combinations of input variables that results in a 1 is TRUE, then the output is 1
 - $F = \text{OR of all input variable combinations that result in a 1}$

Some Definitions

- **Complement:** variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- **Implicant:** product (AND) of literals
 $(A \cdot B \cdot \bar{C}), (\bar{A} \cdot C), (B \cdot \bar{C})$
- **Minterm:** product (AND) that includes **all** input variables
 $(A \cdot B \cdot \bar{C}), (\bar{A} \cdot \bar{B} \cdot C), (\bar{A} \cdot B \cdot \bar{C})$
- **Maxterm:** sum (OR) that includes **all** input variables
 $(A + \bar{B} + \bar{C}), (\bar{A} + B + \bar{C}), (A + B + \bar{C})$

Two-Level Canonical (Standard) Forms

- **Truth table** is the unique **signature** of a Boolean *function* ...
 - But, it is an expensive representation
- A Boolean function can have many alternative Boolean expressions
 - i.e., many alternative Boolean expressions (and gate realizations) may have the same truth table (and function)
 - **If they all say the same thing, why do we care?**
 - Different Boolean expressions lead to different gate realizations
- **Canonical** form: **standard form for a Boolean expression**
 - Provides a unique algebraic signature

Two-Level Canonical Forms: SOP

Sum of Products Form (SOP)

Also known as **disjunctive normal form** or **minterm expansion**

A	B	C	F		0 1 1	1 0 0	1 0 1	1 1 0	1 1 1
0	0	0	0		$\bar{A}BC$	$A\bar{B}\bar{C}$	$A\bar{B}C$	$AB\bar{C}$	ABC
0	0	1	0						
0	1	0	0						
0	1	1	1	←					
1	0	0	1	←					
1	0	1	1	←					
1	1	0	1	←					
1	1	1	1	←					


$F = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$

- Each row in a truth table has a minterm
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)

All Boolean equations can be written in SOP form

Find all the input combinations (minterms) for which the output of the function is TRUE!

SOP Form — Why Does It Work?

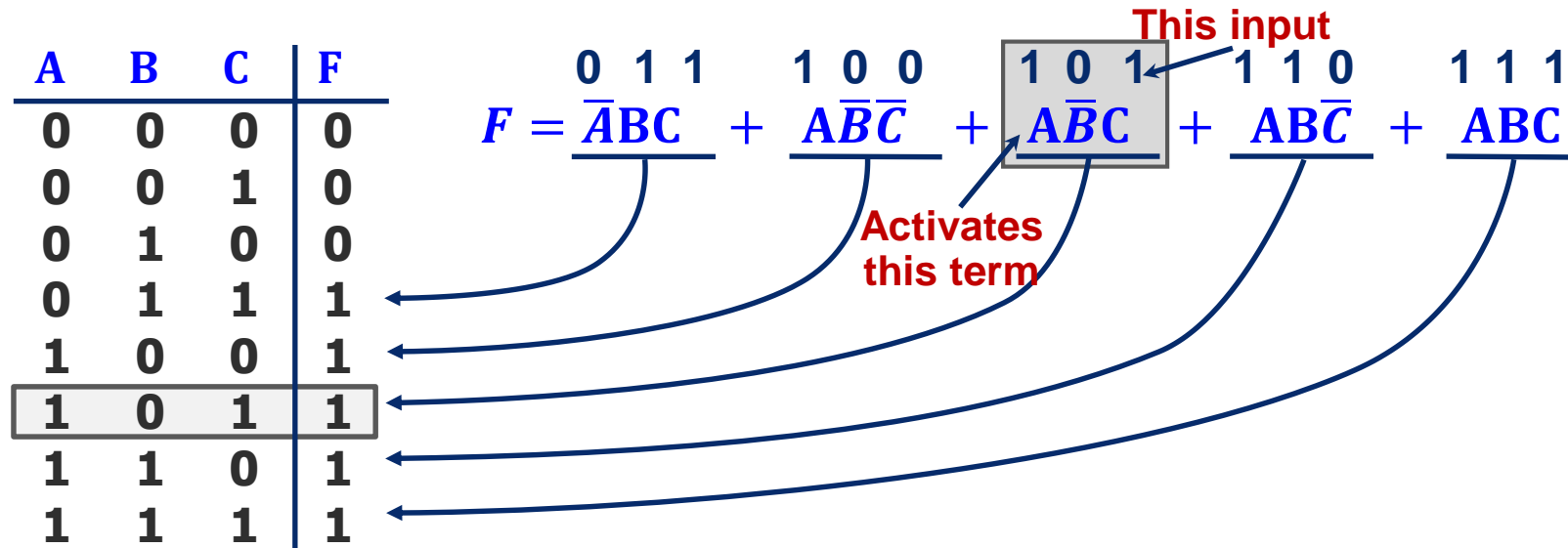

- Only the shaded product term — $\overline{A}BC = 1 \cdot \overline{0} \cdot 1$ — will be 1
- No other product terms will “turn on” — they will all be 0
- So if inputs A B C correspond to a product term in expression,
 - We get $0 + 0 + \dots + 1 + \dots + 0 + 0 = 1$ for output
- If inputs A B C do not correspond to any product term in expression
 - We get $0 + 0 + \dots + 0 = 0$ for output

The function evaluates to TRUE (i.e., output is 1)
 if any of the Products (minterms) causes the output to be 1

Aside: Notation for SOP

- Standard “shorthand” notation
 - If we agree on the **order** of the variables in the rows of truth table...
 - then we can enumerate each row with the decimal number that corresponds to the binary number created by the input pattern

A	B	C	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	1	100 = decimal 4 so this is minterm #4, or m4
1	0	1	1	
1	1	0	1	
1	1	1	1	111 = decimal 7 so this is minterm #7, or m7

f =


We can write this as a sum of products

Or, we can use a summation notation

Canonical SOP Forms

A	B	C	minterms
0	0	0	$\overline{A}\overline{B}\overline{C}$ = m0
0	0	1	$\overline{A}\overline{B}C$ = m1
0	1	0	$\overline{A}B\overline{C}$ = m2
0	1	1	$\overline{A}BC$ = m3
1	0	0	$A\overline{B}\overline{C}$ = m4
1	0	1	$A\overline{B}C$ = m5
1	1	0	$AB\overline{C}$ = m6
1	1	1	ABC = m7

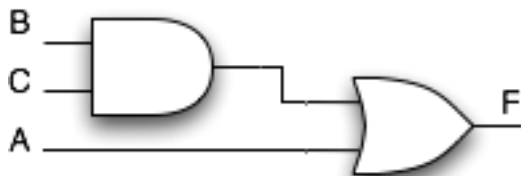Shorthand Notation for
Minterms of 3 Variables



2-Level AND/OR
Realization

F in canonical form:

$$F(A,B,C) = \sum m(3,4,5,6,7) \\ = m3 + m4 + m5 + m6 + m7$$


$F =$

canonical form \neq minimal form

F

From Logic to Gates

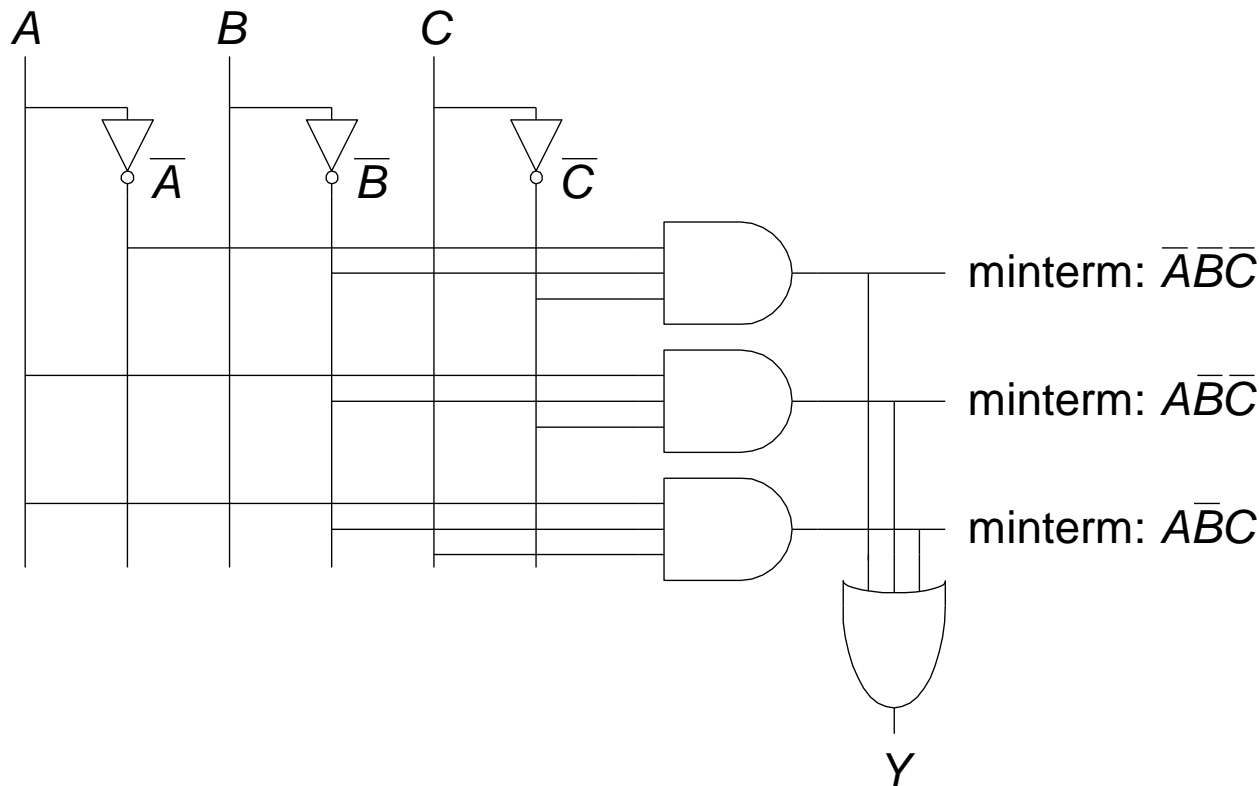- **SOP (sum-of-products) leads to two-level logic**
- Example: $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C)$



Canonical Sum of Products Form: Key Idea

- Any 1-bit function can be represented as a Sum of Products
- A “Product” is the Boolean AND that includes ALL input variables of the function → minterm
- The 1-bit Output of the Function can be represented as
 - Sum (OR) of all minterms that lead to a 1 in the Output
- Logically
 - The function evaluates to TRUE (i.e., output is 1) if ANY of the Products (minterms) causes the Output to be 1
 - SOP form represents the function as the SUM (OR) all Products (minterms) that cause the Output to be 1

Alternative Canonical Form: POS

We can have another canonical form of representation

DeMorgan of SOP of \bar{F}

Product of Sums (POS)

$$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)$$

products

sums

Each sum term represents one of the “**zeros**” of the function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$F = \overset{0}{(A + B + C)} \overset{0}{(A + B + \bar{C})} \overset{1}{(A + \bar{B} + C)}$

This input

Activates this term

For the given input, only the shaded sum term will equal 0


$$A + \bar{B} + C = 0 + \bar{1} + 0$$

Anything ANDed with 0 is 0; Output F will be 0

The function evaluates to FALSE (i.e., output is 0)
if at least one of the Sums (maxterms) causes the output to be 0

Consider $A=0, B=1, C=0$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

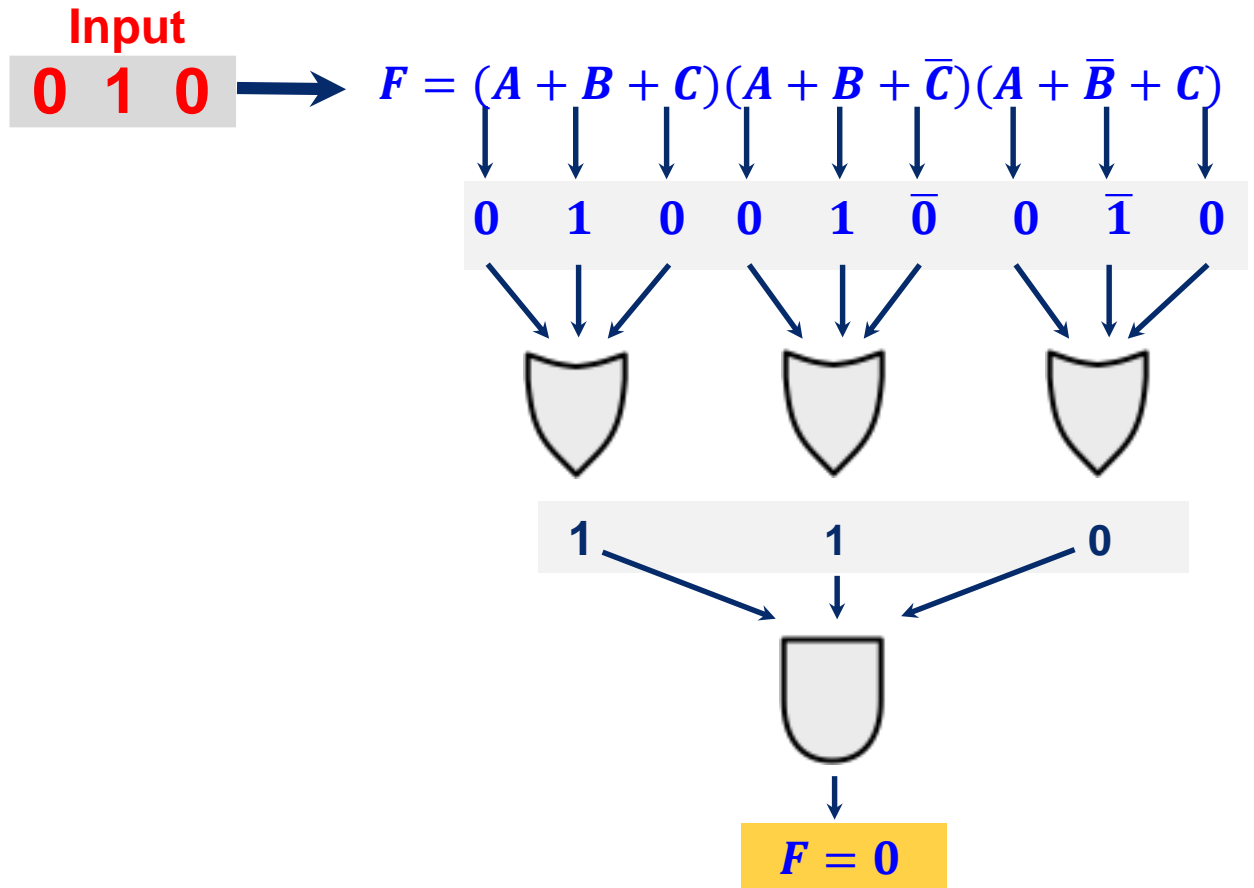

Only one of the products will be 0, anything ANDed with 0 is 0

Therefore, the output is $F = 0$

POS: How to Write It

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)$

$A \quad \bar{B} \quad C$

$A + \bar{B} + C$

Maxterm form:

1. Find truth table rows where F is 0
2. 0 in input col → true literal
3. 1 in input col → complemented literal
4. OR the literals to get a Maxterm
5. AND together all the Maxterms

Or just remember, POS of F is the same as the DeMorgan of SOP of \bar{F} !!

Canonical POS Forms

Product of Sums / Conjunctive Normal Form / Maxterm Expansion

$$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)$$

$$\prod M(0, 1, 2)$$

A	B	C	Maxterms
0	0	0	$A + B + C = M0$
0	0	1	$A + B + \bar{C} = M1$
0	1	0	$A + \bar{B} + C = M2$
0	1	1	$A + \bar{B} + \bar{C} = M3$
1	0	0	$\bar{A} + B + C = M4$
1	0	1	$\bar{A} + B + \bar{C} = M5$
1	1	0	$\bar{A} + \bar{B} + C = M6$
1	1	1	$\bar{A} + \bar{B} + \bar{C} = M7$

Maxterm shorthand notation
for a function of three variables

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Note that you
form the
maxterms around
the “zeros” of the
function

This is **not** the
complement of
the function!

Useful Conversions

1. **Minterm to Maxterm conversion:**

rewrite minterm shorthand using maxterm shorthand
replace minterm indices with the indices not already used

E.g., $F(A, B, C) = \sum m(3, 4, 5, 6, 7) = \prod M(0, 1, 2)$

2. **Maxterm to Minterm conversion:**

rewrite maxterm shorthand using minterm shorthand
replace maxterm indices with the indices not already used

E.g., $F(A, B, C) = \prod M(0, 1, 2) = \sum m(3, 4, 5, 6, 7)$

3. **Expansion of F to expansion of \bar{F} :**

$$\begin{array}{ll} \text{E. g., } F(A, B, C) = \sum m(3, 4, 5, 6, 7) & \longrightarrow \bar{F}(A, B, C) = \sum m(0, 1, 2) \\ = \prod M(0, 1, 2) & \longrightarrow = \prod M(3, 4, 5, 6, 7) \end{array}$$

4. **Minterm expansion of F to Maxterm expansion of \bar{F} :**

rewrite in Maxterm form, using the same indices as F


$$\begin{array}{ll} \text{E. g., } F(A, B, C) = \sum m(3, 4, 5, 6, 7) & \longrightarrow \bar{F}(A, B, C) = \prod M(3, 4, 5, 6, 7) \\ = \prod M(0, 1, 2) & \longrightarrow = \sum m(0, 1, 2) \end{array}$$

Logic Simplification (or Minimization)

- Using Boolean Algebra, we can simplify the SOP or POS form of any function in a methodical way
- Starting with the canonical SOP or POS form enables convenience and automation
 - Truth table \rightarrow SOP/POS form \rightarrow Boolean Simplification Rules
- **Example (full 1-bit adder – more later):**

$$S = F(A, B, C_{in})$$

$$C_{out} = G(A, B, C_{in})$$

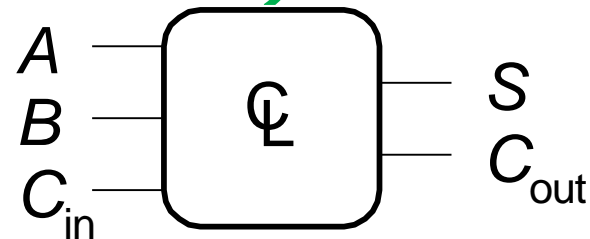


$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

Logic Simplification Example: SOP Form


- **SOP (sum-of-products) form of function Y**

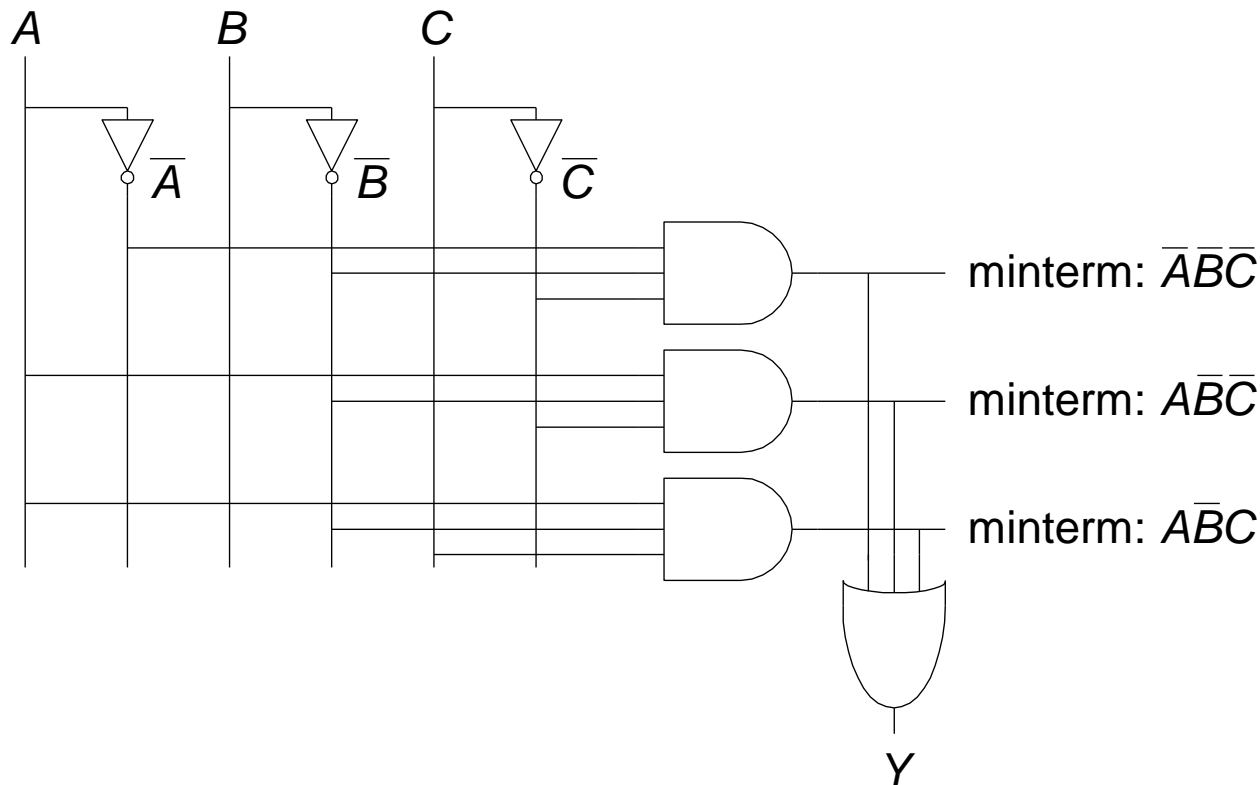- Example: $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C)$



Logic Simplification Example: Simplified

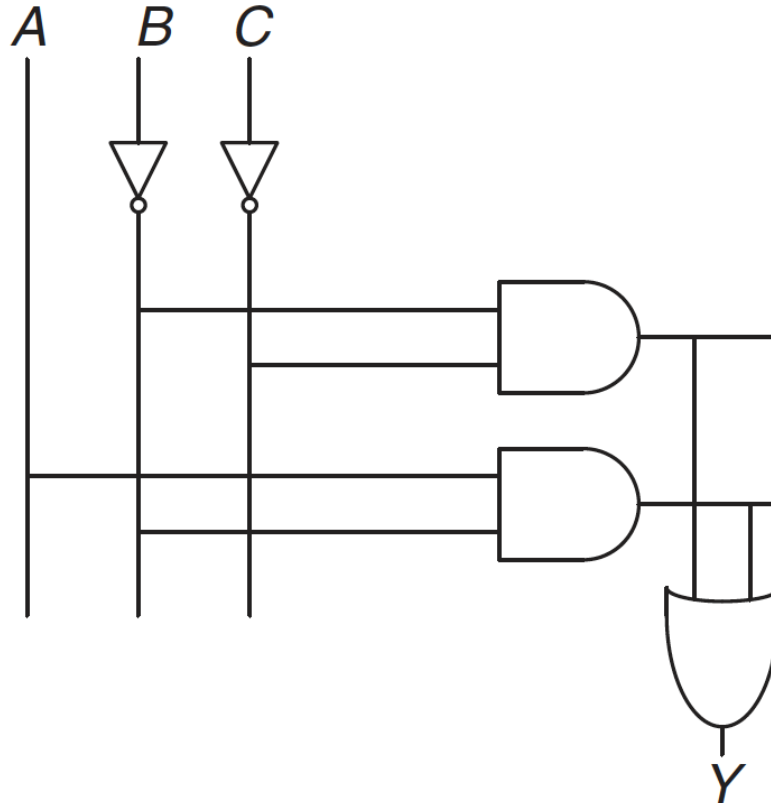- **SOP (sum-of-products) form of function Y**
- Example: $Y = (\overline{B} \cdot \overline{C}) + (A \cdot \overline{B})$



Let's Cover Some Basic Combinational Blocks

Combinational Building Blocks used in Modern Computers

Combinational Building Blocks


- Combinational logic is often grouped into larger building blocks to build more **complex systems**
 - Hides the **unnecessary gate-level details** to emphasize the function of the building block
 - We now look at:
 - Decoder
 - Multiplexer
 - Full adder
 - PLA (Programmable Logic Array)
-

Decoder

Decoder



- “Input pattern detector”
- n inputs and 2^n outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The **one output** that is logically 1 is the output corresponding to the input **pattern** that the logic circuit is expected to detect
- Example: 2-to-4 decoder

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

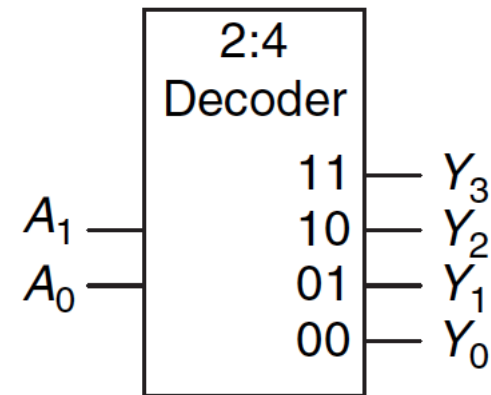


Decoder (I)

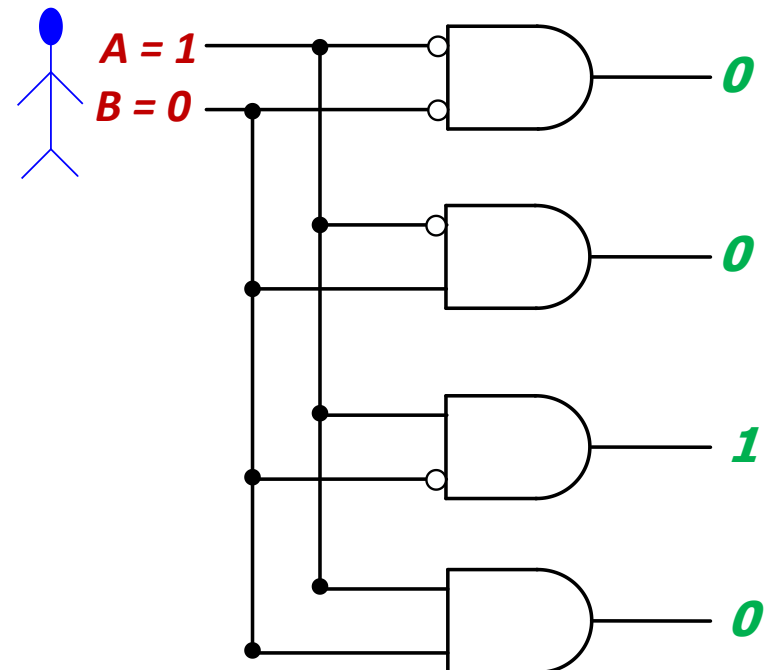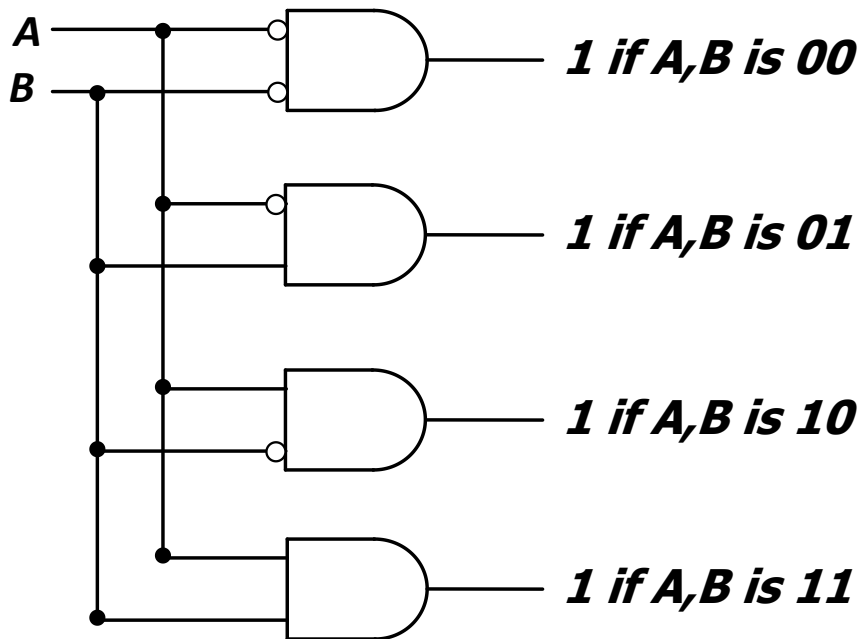- n inputs and 2^n outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The **one output** that is logically 1 is the output corresponding to the input **pattern** that the logic circuit is expected to detect



Decoder (II)

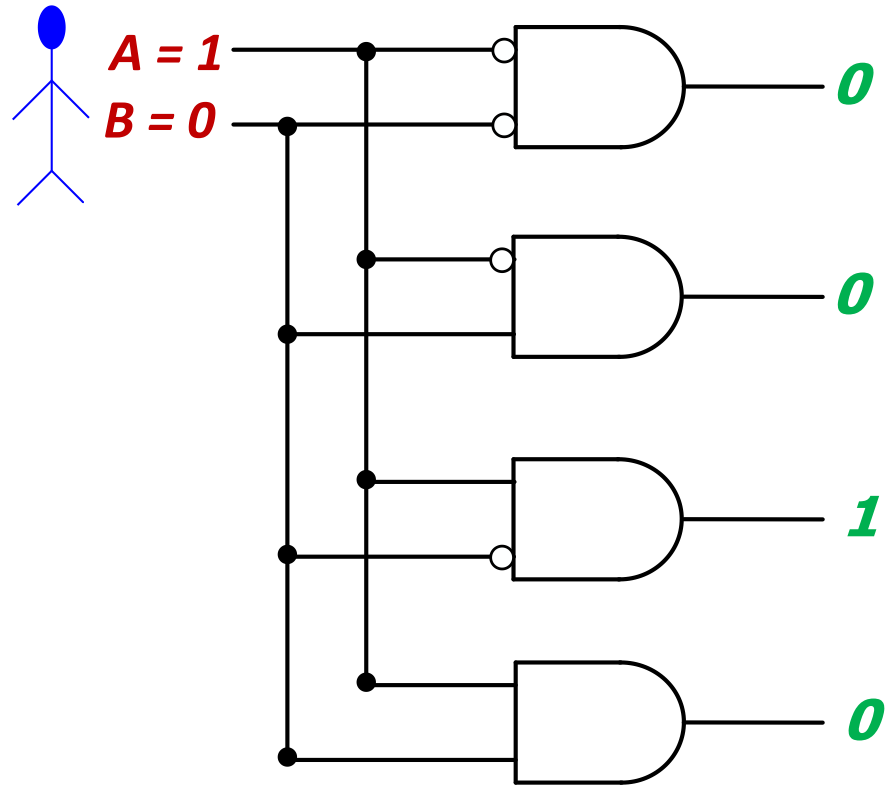- The decoder is useful in determining how to interpret a bit pattern
 - **It could be the address of a row in DRAM, that the processor intends to read from**
 - **It could be an instruction in the program and the processor has to decide what action to do! (based on *instruction opcode*)**




Multiplexer (MUX)

Multiplexer (MUX), or Selector



- **Selects** one of the N inputs to connect it to the output
 - based on the value of a $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX

S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

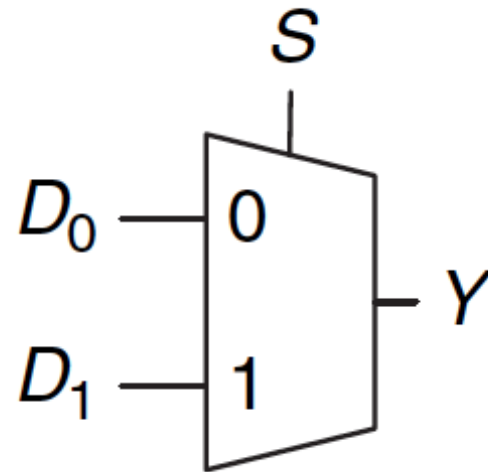

Multiplexer (MUX), or Selector (II)

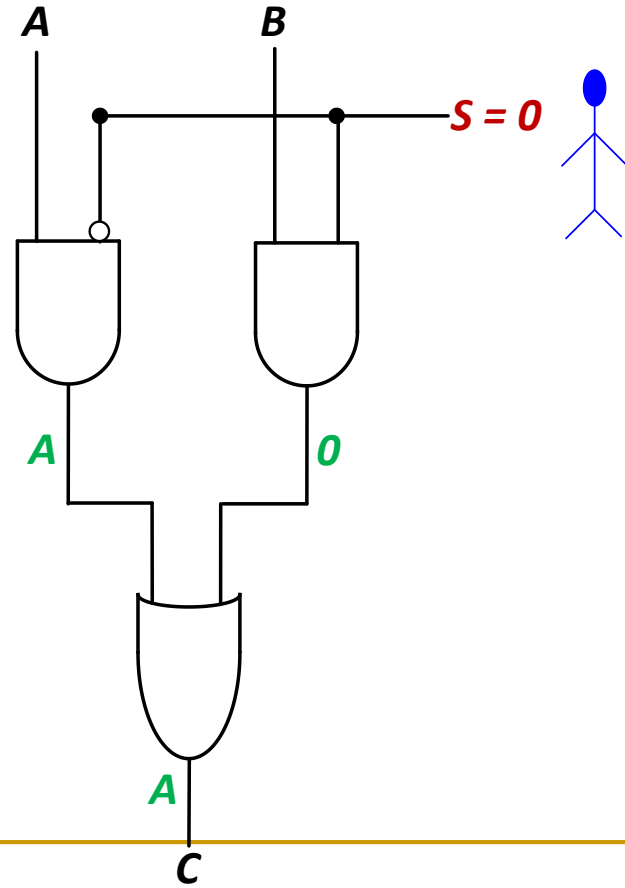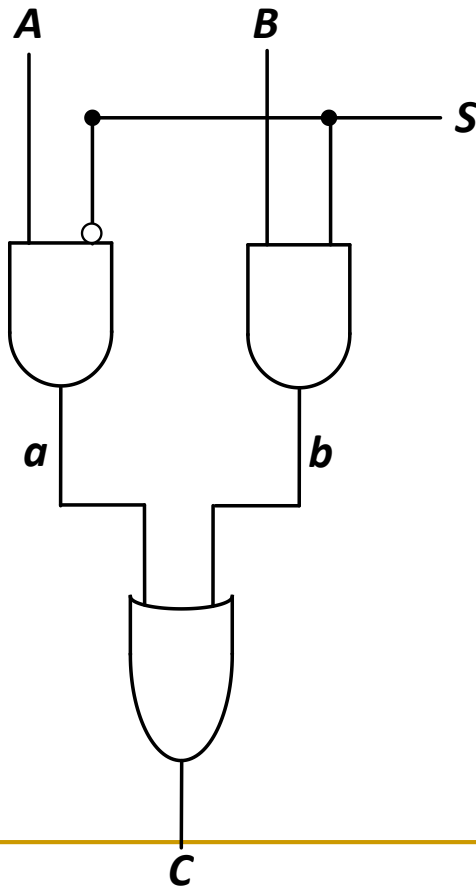
- **Selects** one of the N inputs to connect it to the output
 - based on the value of a $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX



Multiplexer (MUX), or Selector (III)



- The output C is always connected to either the input A or the input B
 - Output value depends on the value of the **select line S**

S	C
0	A
1	B

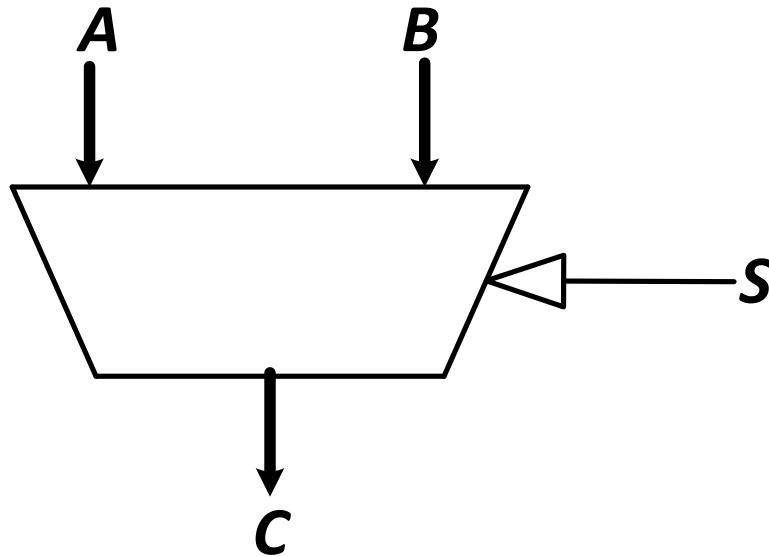

- **Your task:** Draw the schematic for an 4-input (4:1) MUX
 - Gate level: as a combination of basic AND, OR, NOT gates
 - Module level: As a combination of 2-input (2:1) MUXes

A 4-to-1 Multiplexer

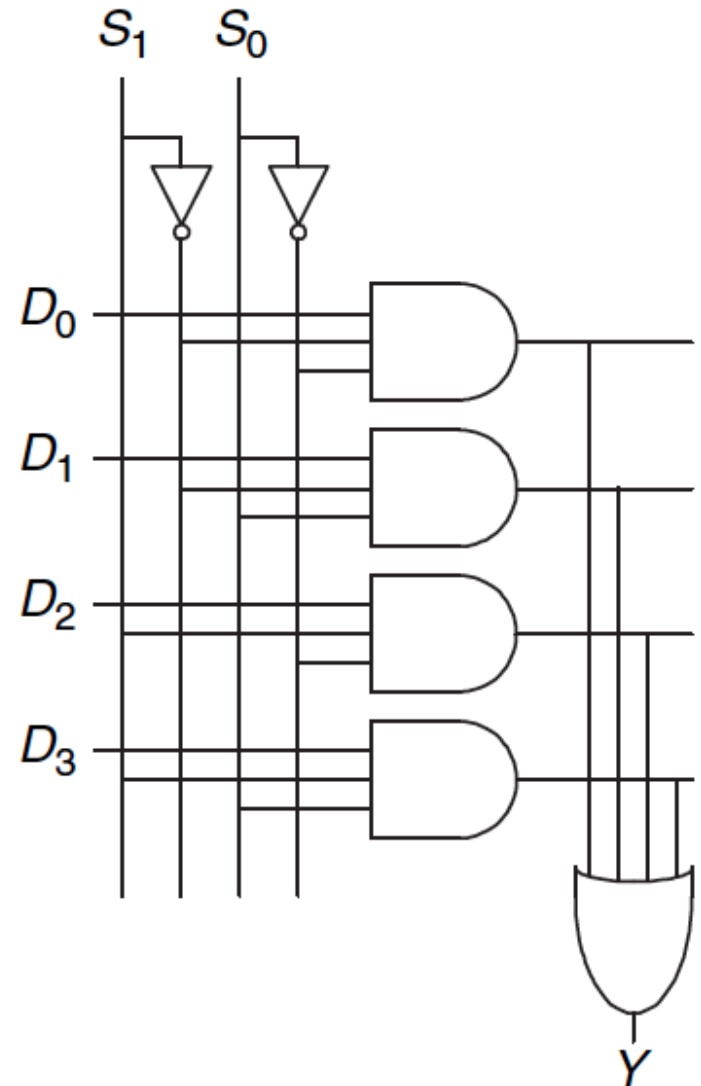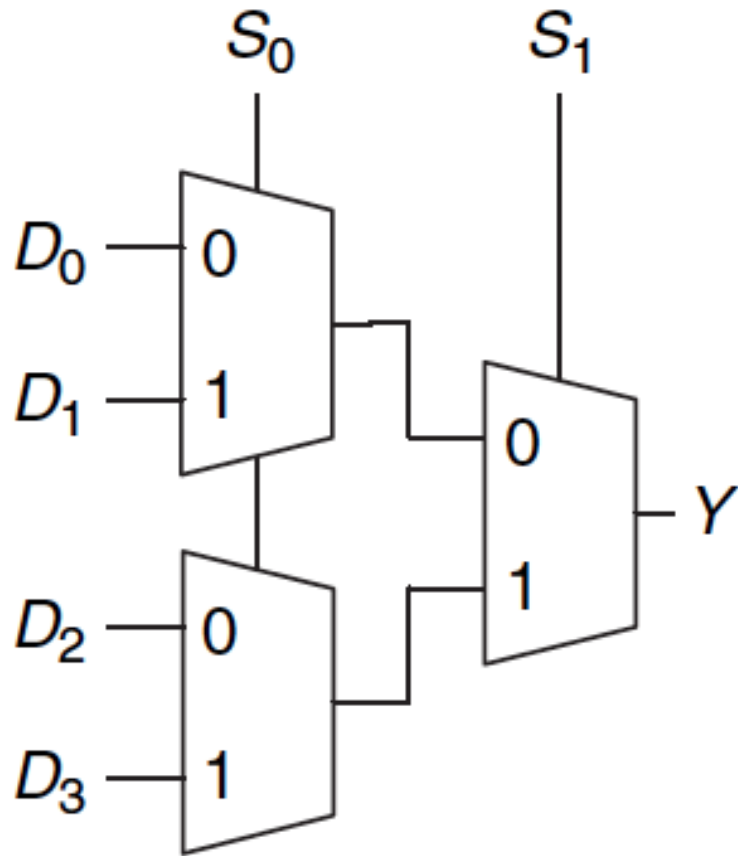

Full Adder

Full Adder (I)

■ Binary addition

- Similar to decimal addition
- From right to left
- One column at a time
- One sum and one carry bit

$$\begin{array}{r}
 a_{n-1}a_{n-2} \dots a_1a_0 \\
 b_{n-1}b_{n-2} \dots b_1b_0 \\
 \underline{C_n C_{n-1} \dots C_1} \\
 S_{n-1} \dots S_1S_0
 \end{array}$$

↓


- Truth table of binary addition on **one column** of bits within two n-bit operands

a_i	b_i	$carry_i$	$carry_{i+1}$	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder (II)

■ Binary addition

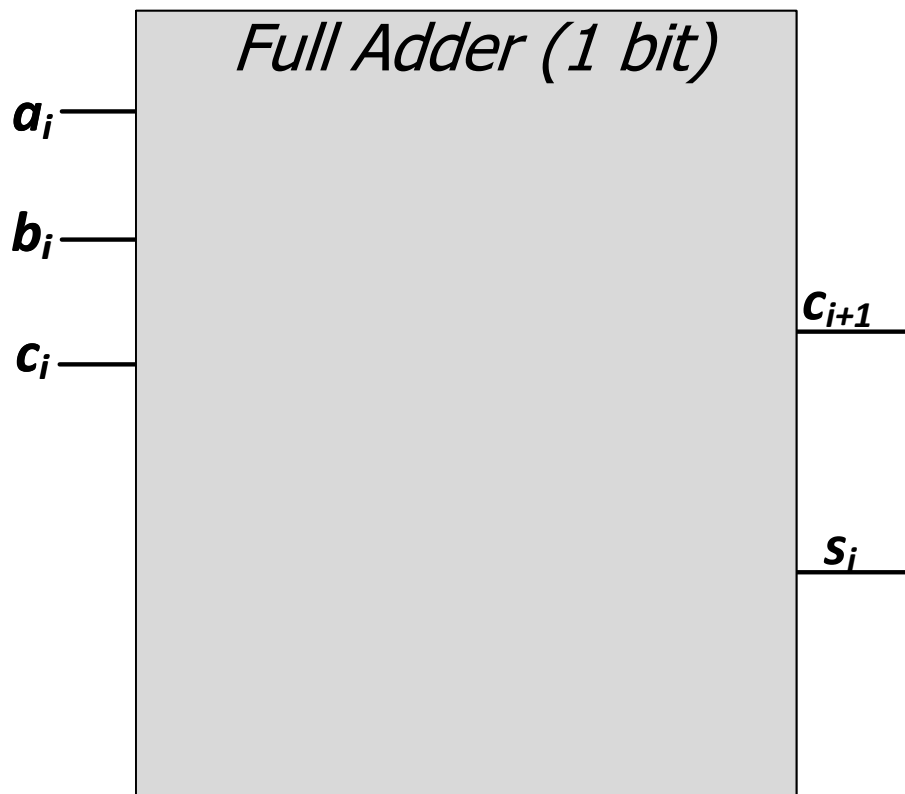- N 1-bit additions
- **SOP of 1-bit addition**




$$\begin{array}{r} a_{n-1}a_{n-2} \dots a_1a_0 \\ b_{n-1}b_{n-2} \dots b_1b_0 \\ \hline C_n C_{n-1} \dots C_1 \\ \hline S_{n-1} \dots S_1S_0 \end{array}$$

A vertical arrow points downwards from the right side of the addition, indicating the progression of bits from a_0 to a_{n-1} .

a_i	b_i	$carry_i$	$carry_{i+1}$	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

4-Bit Adder from Full Adders

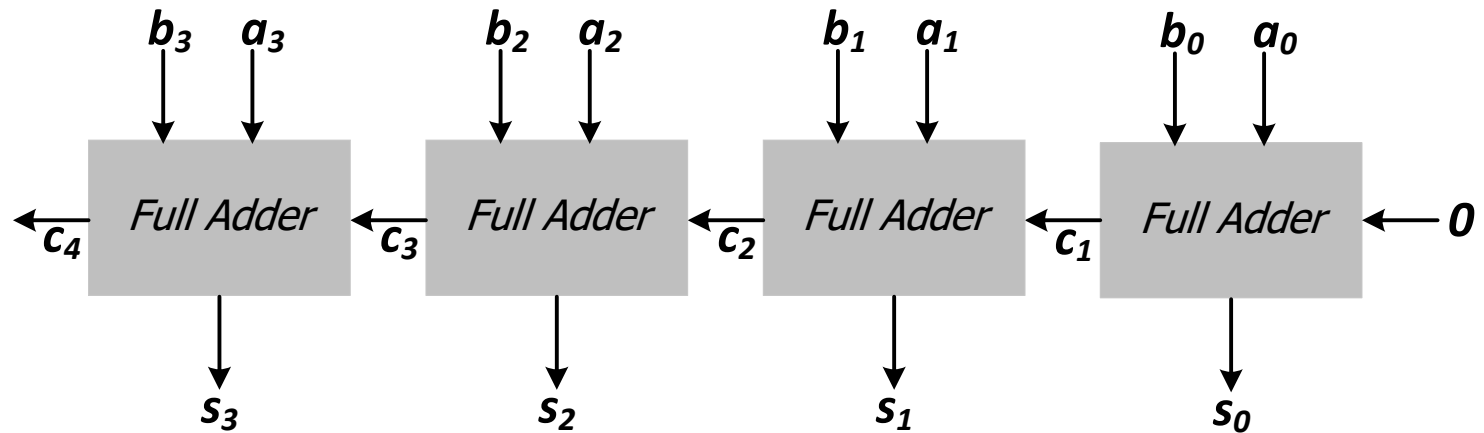- Creating a **4-bit adder** out of 1-bit full adders
 - To add two 4-bit binary numbers A and B



$$\begin{array}{rcccc} & a_3 & a_2 & a_1 & a_0 \\ + & b_3 & b_2 & b_1 & b_0 \\ \hline c_4 & c_3 & c_2 & c_1 & \\ \hline s_3 & s_2 & s_1 & s_0 & \end{array}$$

$$\begin{array}{rcccc} & 1 & 0 & 1 & 1 \\ + & 1 & 0 & 0 & 1 \\ \hline 1 & 0 & 1 & 1 & \\ \hline 0 & 1 & 0 & 0 & \end{array}$$

Adder Design: Ripple Carry Adder



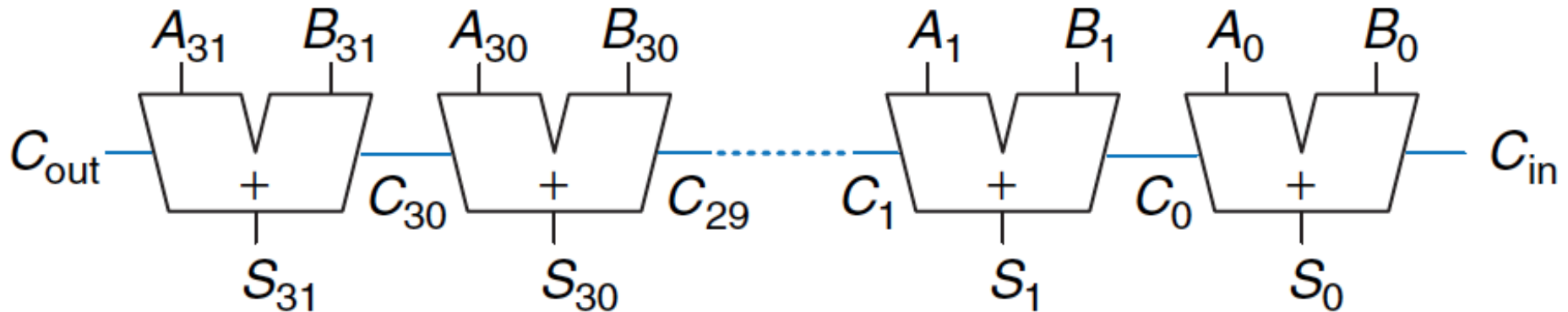


Figure 5.5 32-bit ripple-carry adder

Adder Design: Carry Lookahead Adder

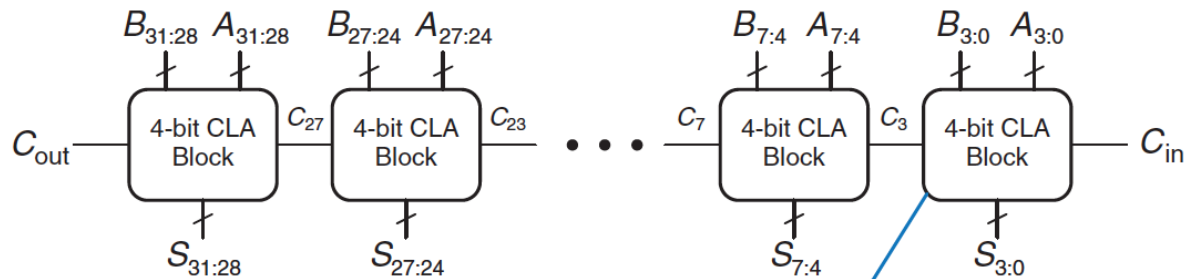

(a)

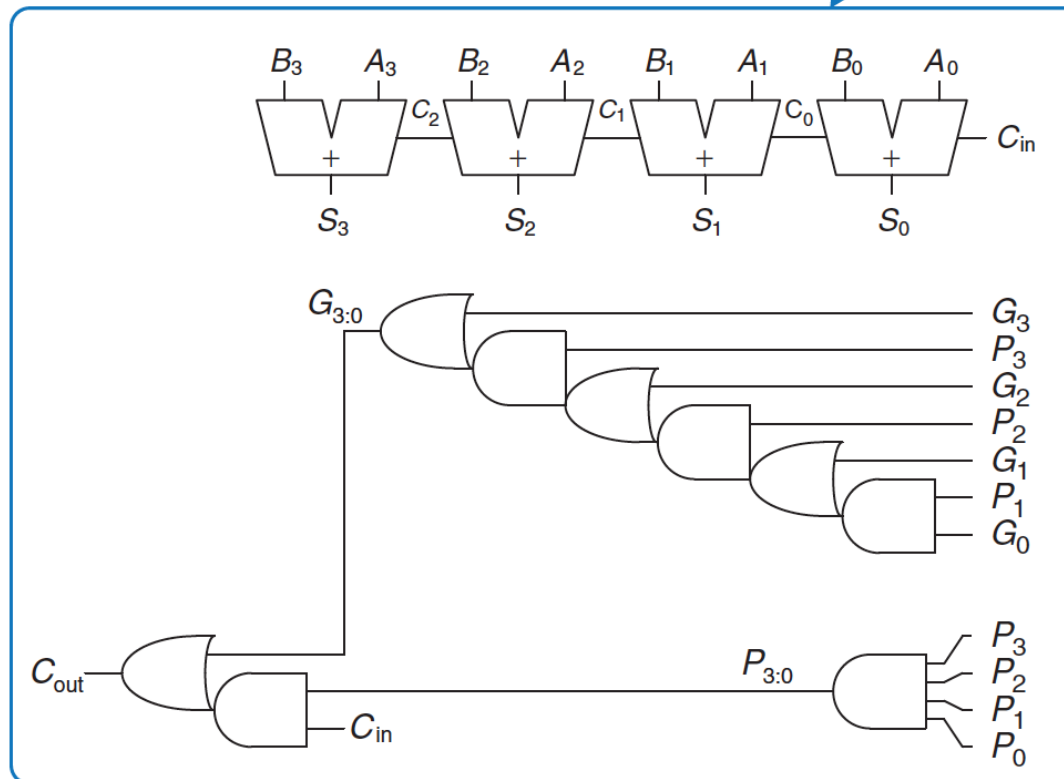


(b)

Programmable Logic Array (PLA)

PLA: Recall: From Logic to Gates

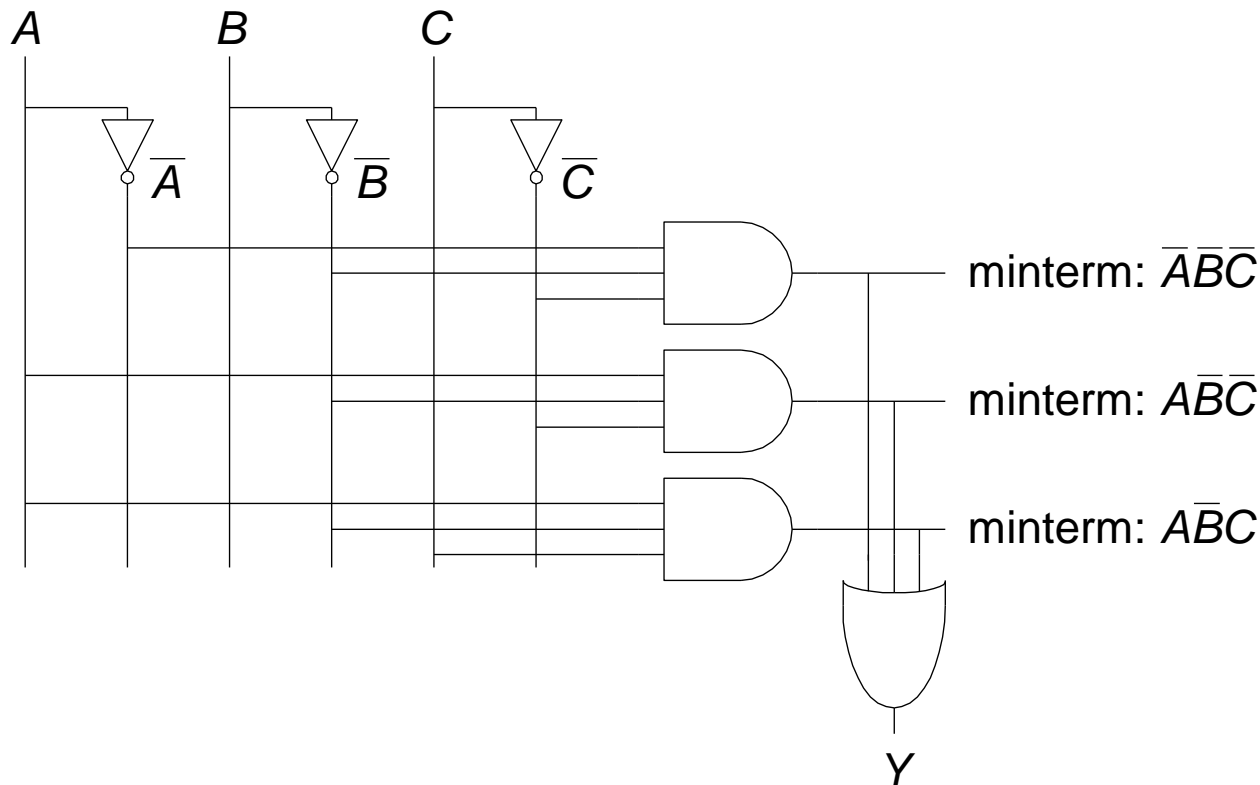- **SOP (sum-of-products) leads to two-level logic**
- Example: $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C)$



The Programmable Logic Array (PLA)


- The below logic structure is a very **common** building block for implementing any collection of logic functions one wishes to

- An **array** of AND gates followed by an **array** of OR gates
- **How do we determine the number of AND gates?**

- **Remember SOP:** the number of possible minterms


- For an n -input logic function, we need a PLA with 2^n n -input AND gates

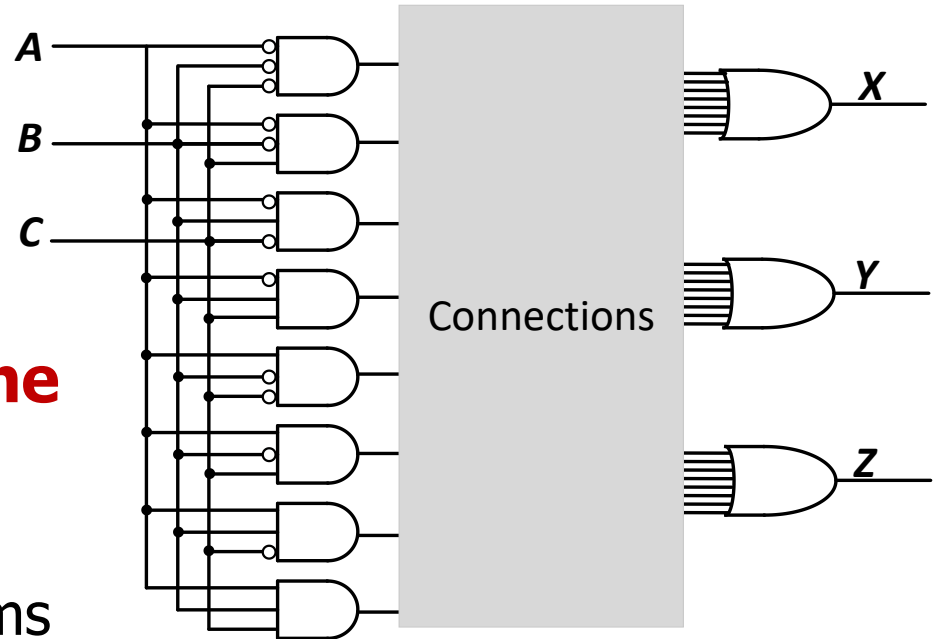- **How do we determine the number of OR gates?** The number of output columns in the truth table




The Programmable Logic Array (PLA)


- How do we implement a logic function?
 - Connect the output of an AND gate to the input of an OR gate if the corresponding minterm is included in the SOP
 - This is a simple programmable logic construct
- **Programming a PLA:** we program the connections from AND gate outputs to OR gate inputs to implement a desired logic function
- Have you seen any other type of programmable logic?
 - Yes! An FPGA...
 - An FPGA uses more advanced structures, as we saw in Lecture 3

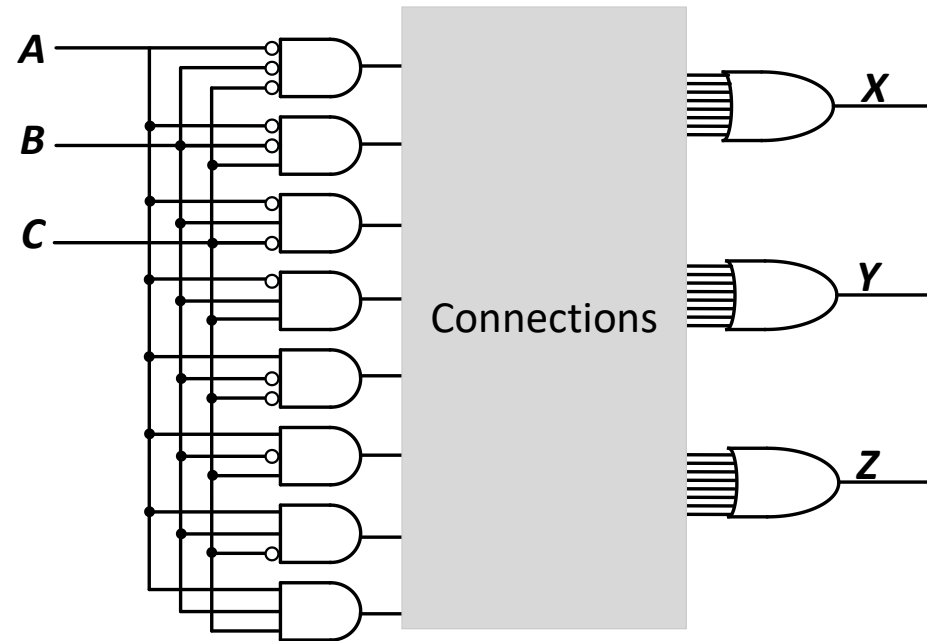


PLA Example (I)

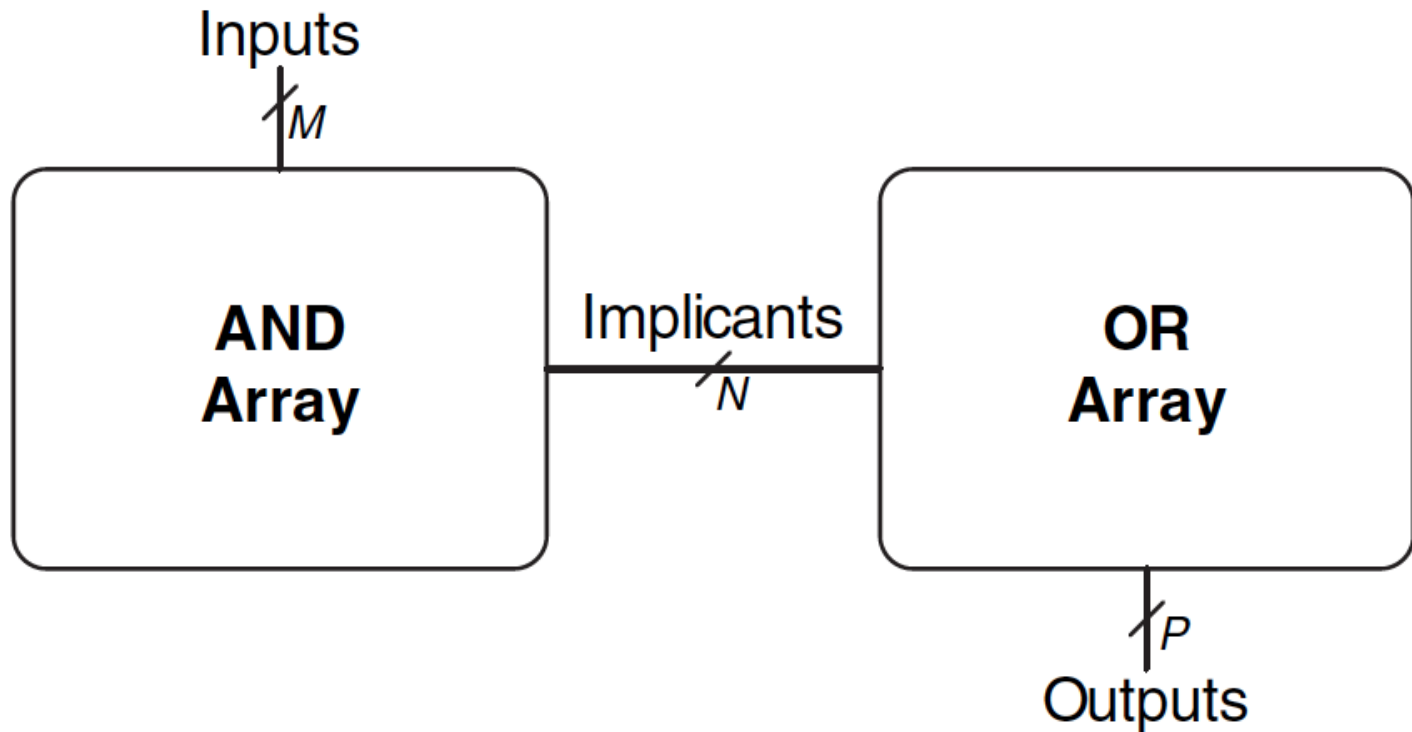


PLA Example Function (II)

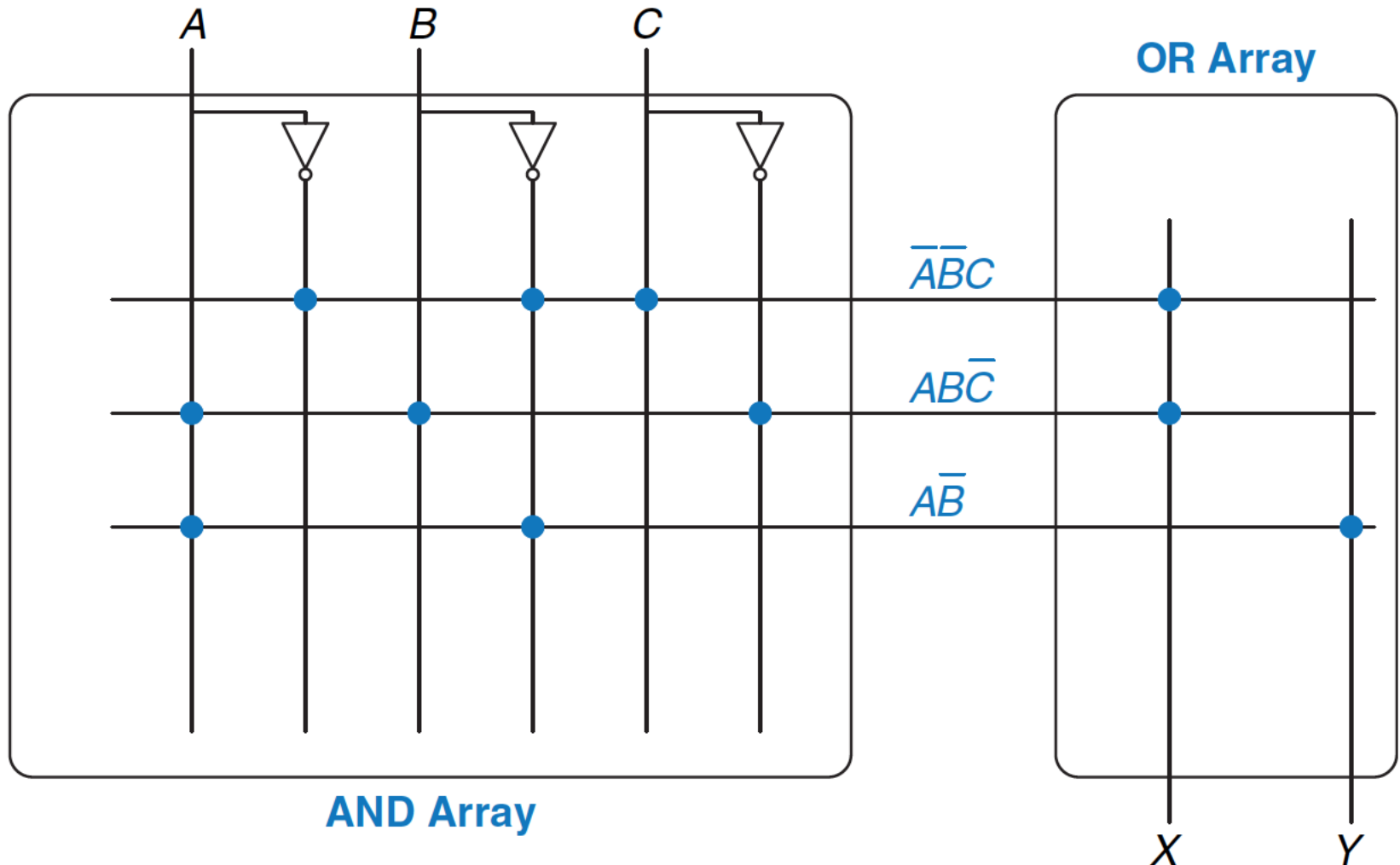

PLA Example Function (III)

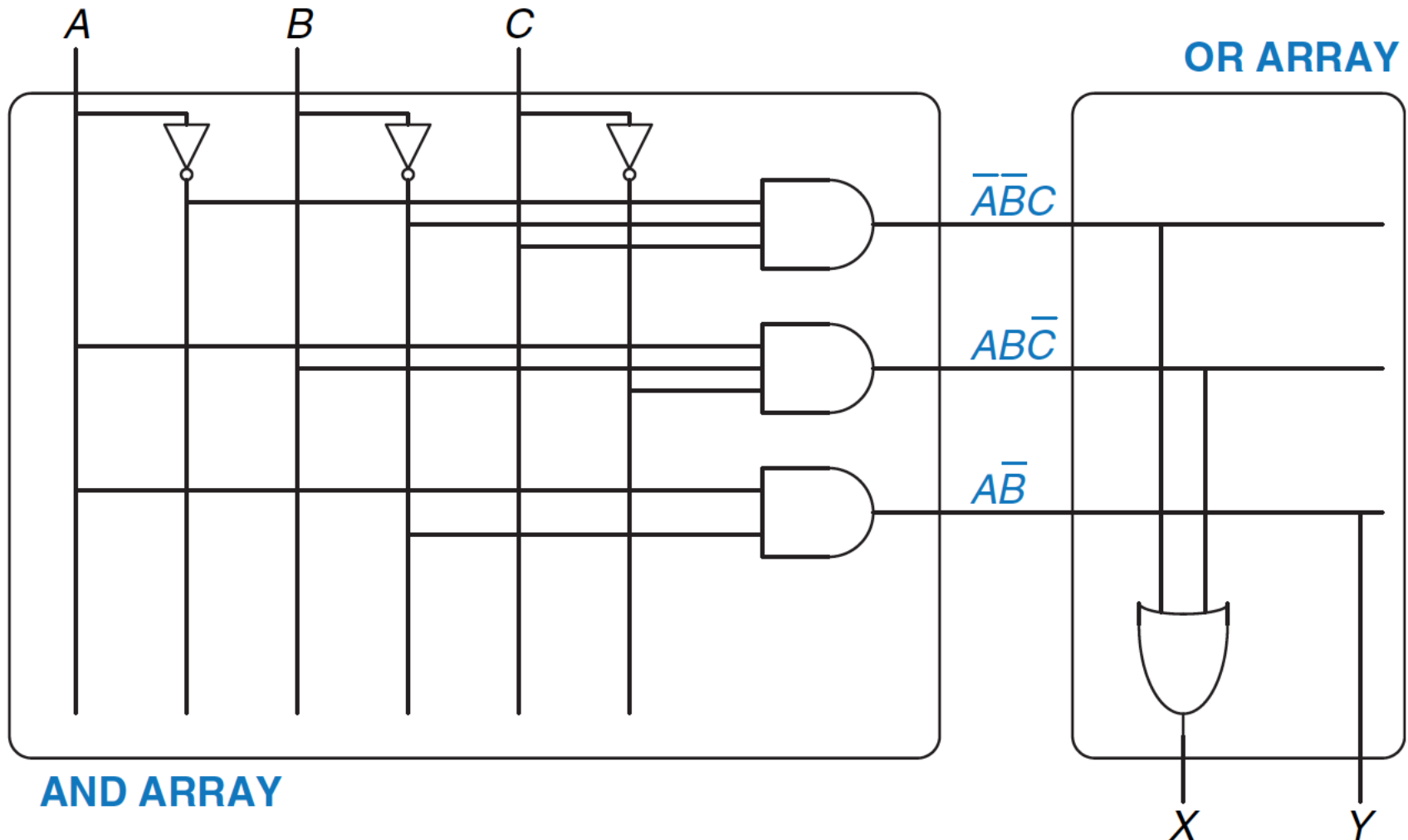

Implementing a Full Adder Using a PLA

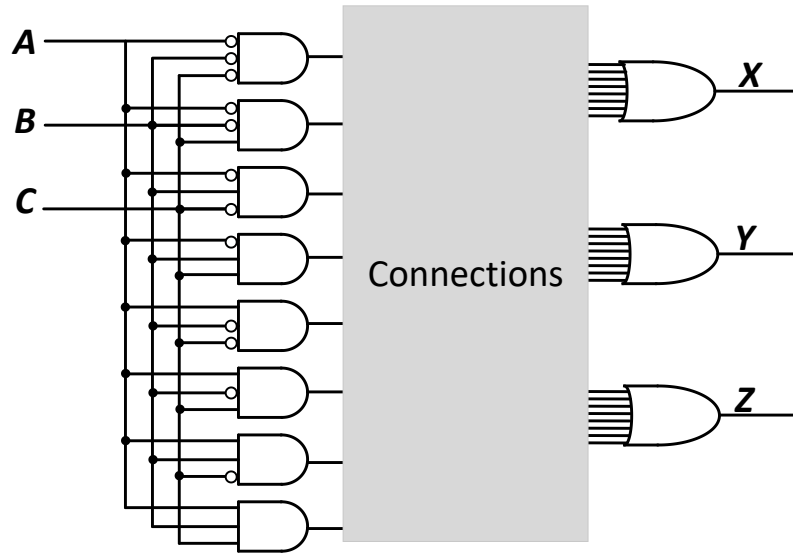


Truth table of a full adder

a_i	b_i	$carry_i$	$carry_{i+1}$	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

This input should not be connected to any outputs

We do not need this output

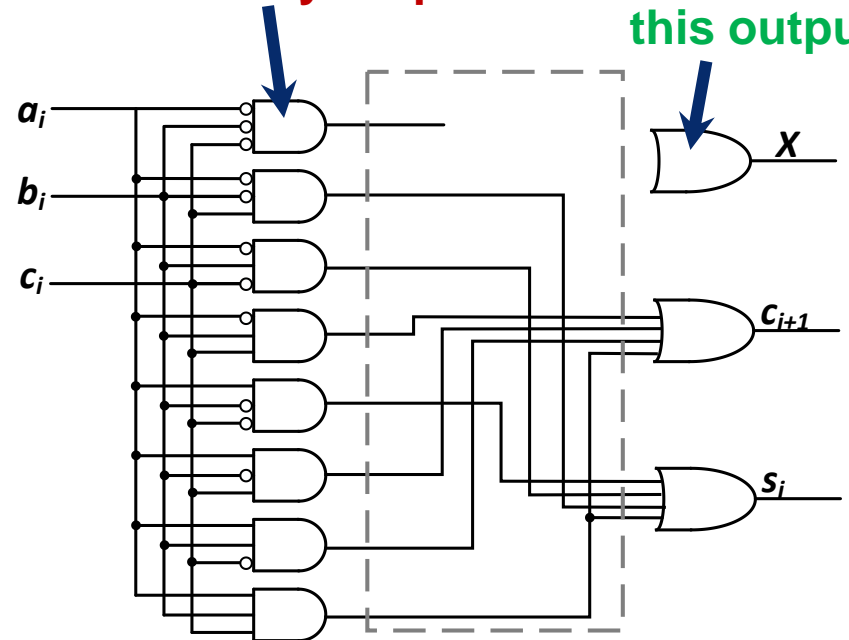

Logical Completeness

Logical (Functional) Completeness

- **Any logic function** we wish to implement could be accomplished with a PLA
 - PLA consists of **only** AND gates, OR gates, and inverters
 - We just have to program connections based on SOP of the intended logic function
- The set of gates {AND, OR, NOT} is **logically complete** because we can build a circuit to carry out the specification of **any truth table** we wish, without using any other kind of gate
- NAND is also logically complete. So is NOR.
 - **Your task:** Prove this.

More Combinational Blocks



More Combinational Building Blocks

- H&H Chapter 2 in full
 - Required Reading
 - E.g., see Tri-state Buffer and Z values in Section 2.6
- H&H Chapter 5
 - Will be required reading soon.
- You will benefit greatly by reading the “combinational” parts of Chapter 5 soon.
 - Sections 5.1 and 5.2

Comparator

Equality Checker (Compare if Equal)

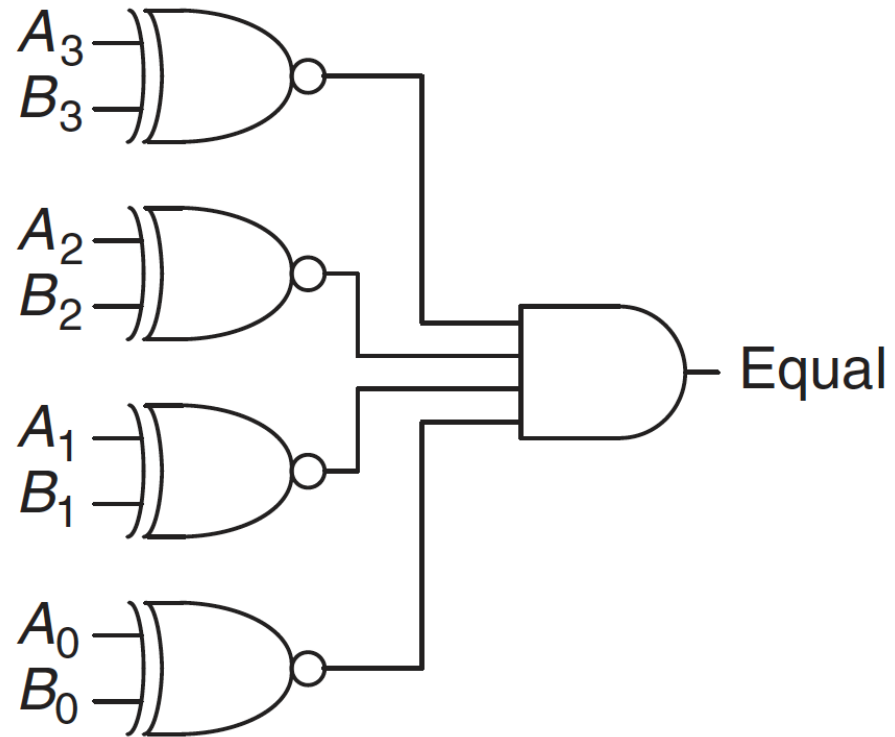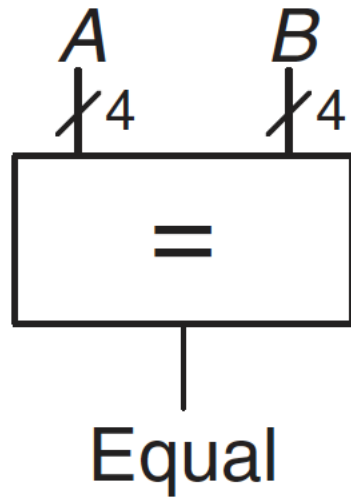- Checks if two N-input values are exactly the same
- Example: 4-bit Comparator



ALU (Arithmetic Logic Unit)

ALU (Arithmetic Logic Unit)

- Combines a variety of arithmetic and logical operations into a single unit (that performs only one function at a time)
- Usually denoted with this symbol:

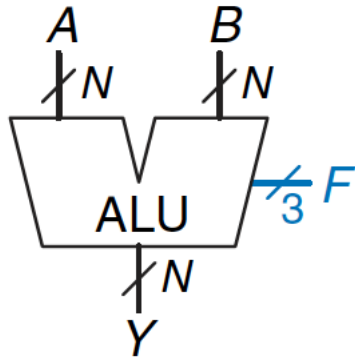


Figure 5.14 ALU symbol


Table 5.1 ALU operations

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT

Example ALU (Arithmetic Logic Unit)

Table 5.1 ALU operations

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \overline{B}
101	A OR \overline{B}
110	A – B
111	SLT

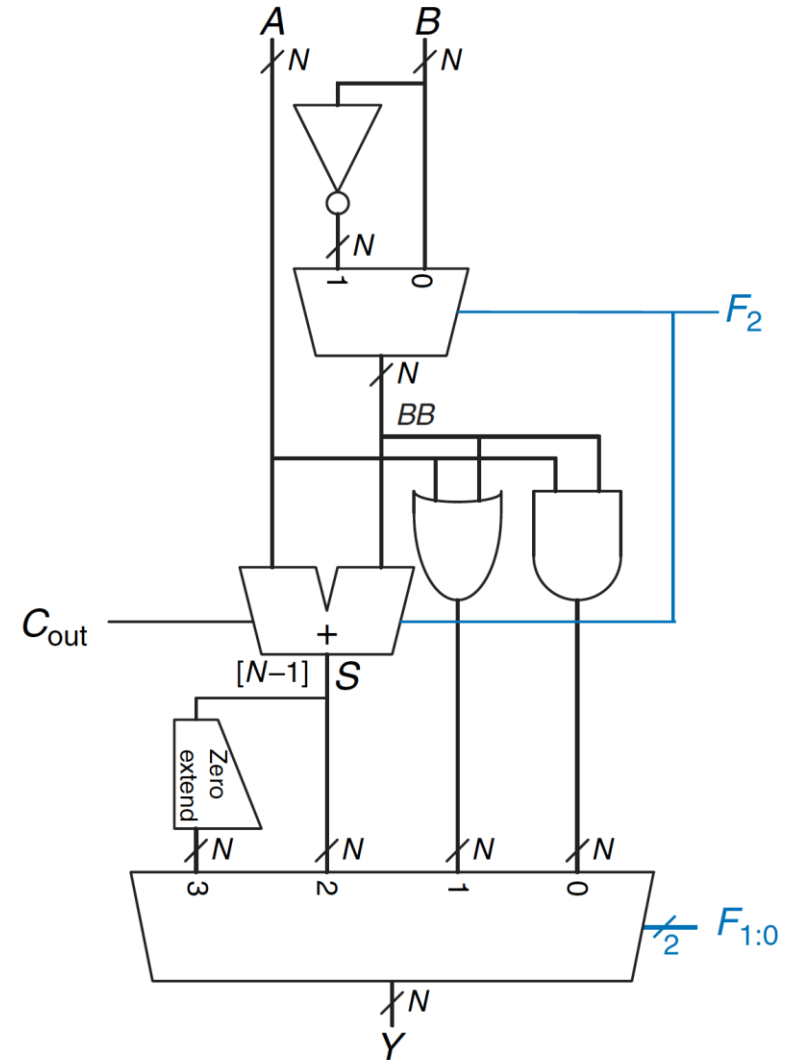

More Combinational Building Blocks

- See H&H Chapter 5.2 for
 - Subtractor (using 2's Complement Representation)
 - Shifter and Rotator
 - Multiplier
 - Divider
 - ...

More Combinational Building Blocks

- H&H Chapter 2 in full
 - Required Reading
 - E.g., see Tri-state Buffer and Z values in Section 2.6
- H&H Chapter 5
 - Will be required reading soon.
- You will benefit greatly by reading the “combinational” parts of Chapter 5 soon.
 - Sections 5.1 and 5.2

Tri-State Buffer

Tri-State Buffer

- A tri-state buffer enables gating of different signals onto a wire

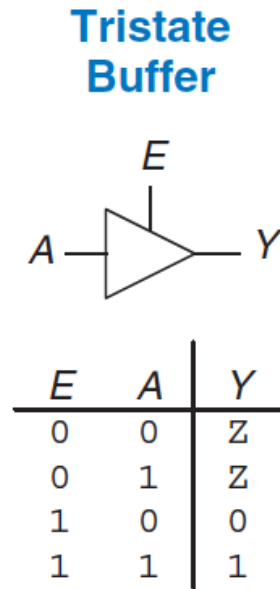



Figure 2.40 Tristate buffer

- **Floating signal (Z):** Signal that is not driven by any circuit
 - Open circuit, floating wire


Example: Use of Tri-State Buffers

- Imagine a wire connecting the CPU and memory
 - At any time only the CPU or the memory can place a value on the wire, both not both
 - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time


Example Design with Tri-State Buffers

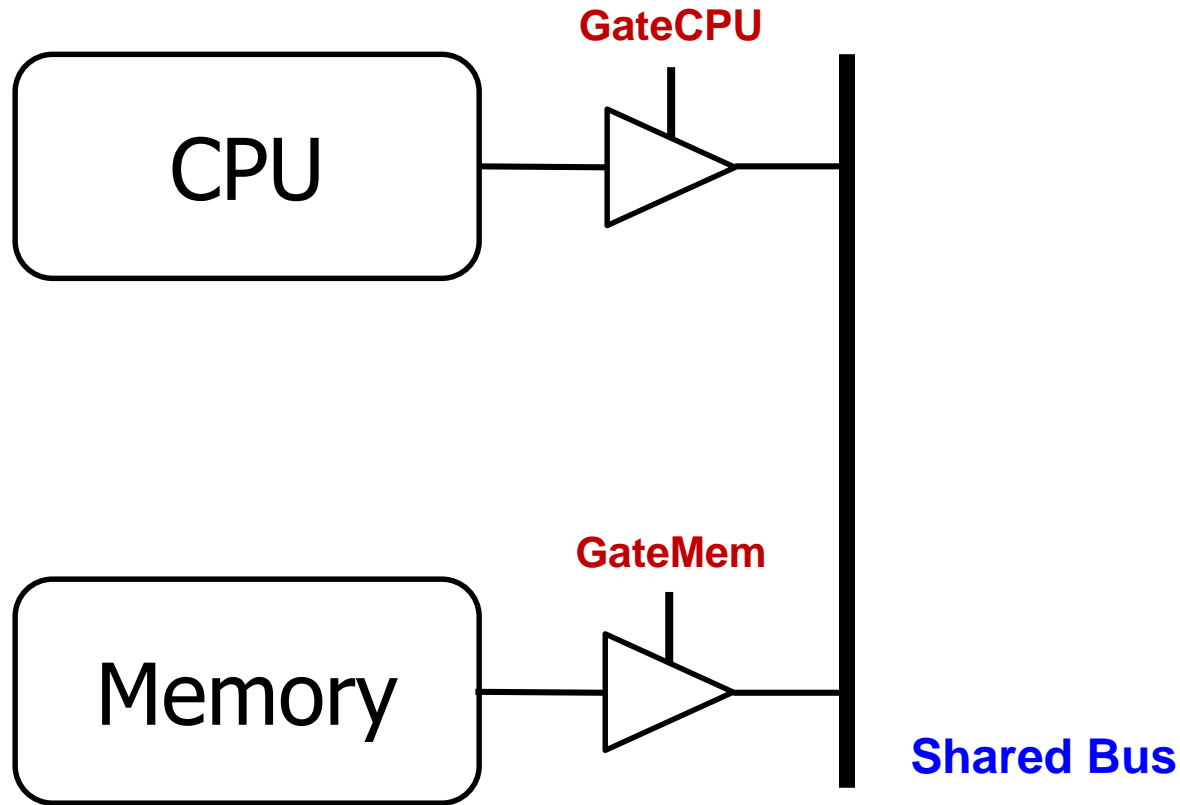

Another Example

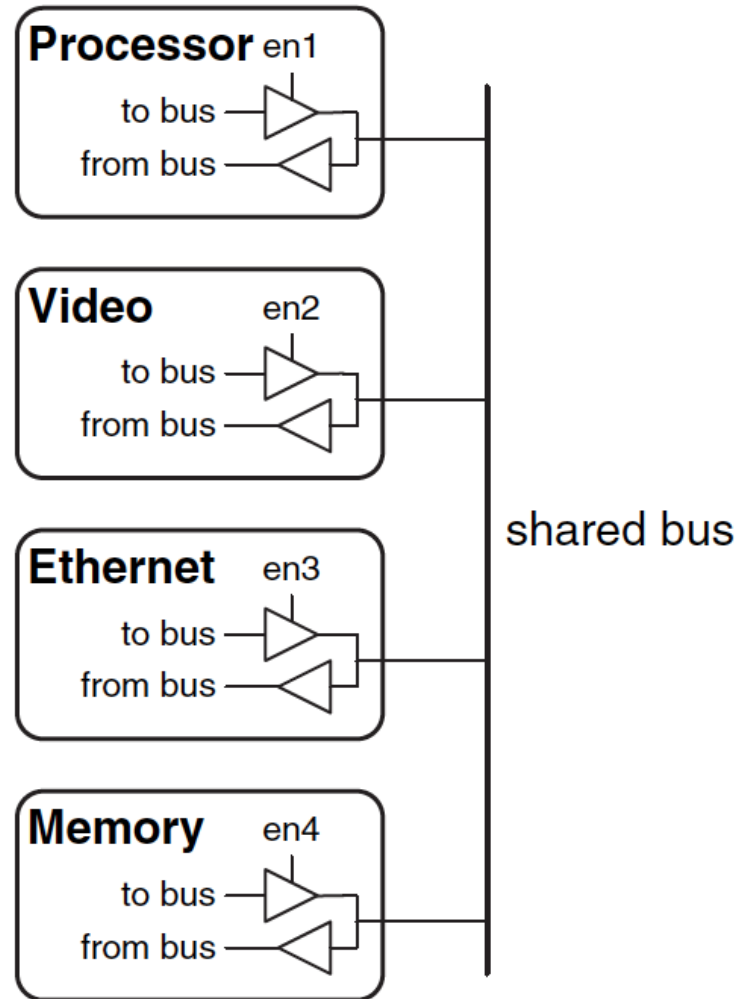


Multiplexer Using Tri-State Buffers

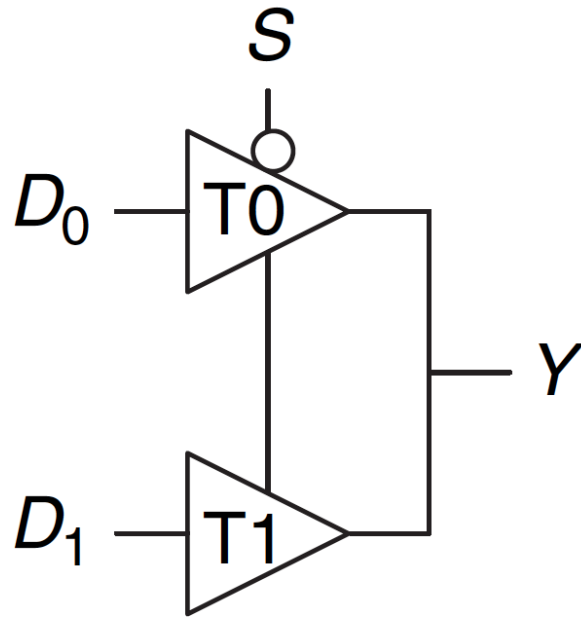

$$Y = D_0 \bar{S} + D_1 S$$

Figure 2.56 Multiplexer using tristate buffers

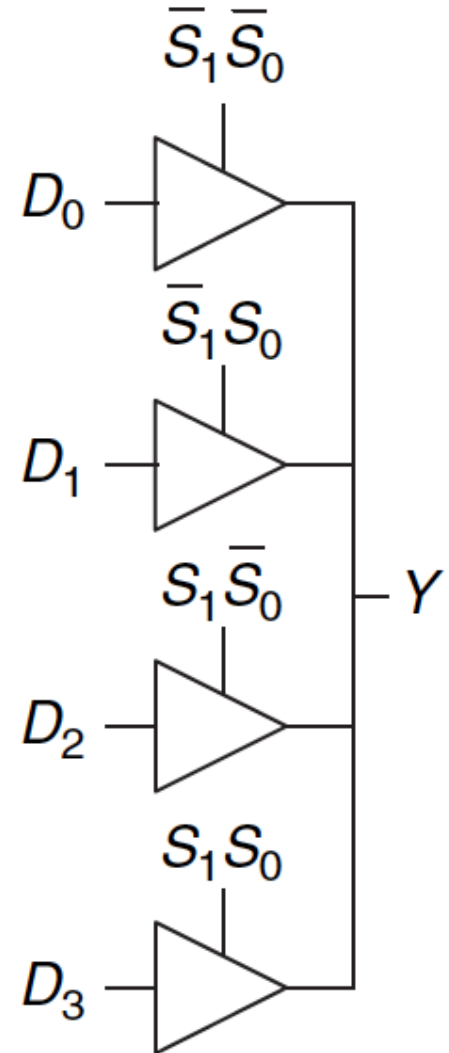

Aside: Logic Using Multiplexers

- Multiplexers can be used as lookup tables to perform logic functions


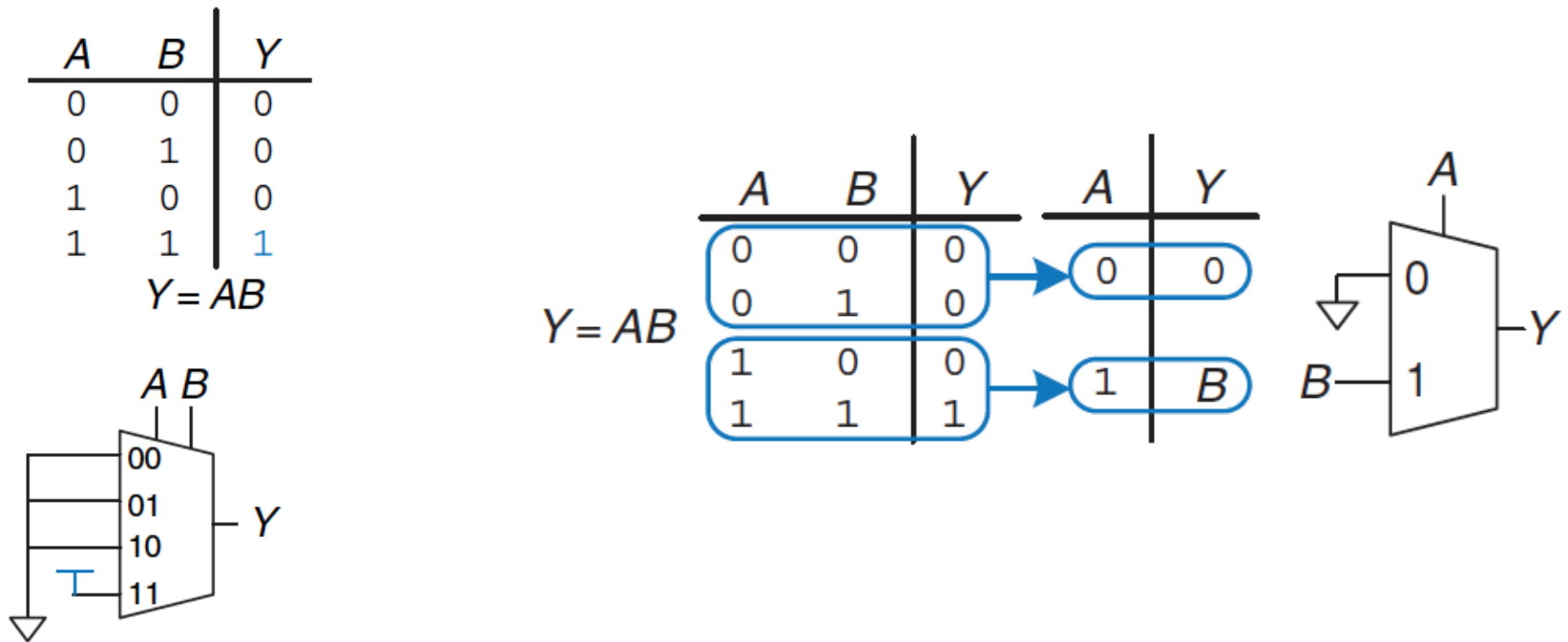


Figure 2.59 4:1 multiplexer implementation of two-input AND function

Aside: Logic Using Multiplexers (II)

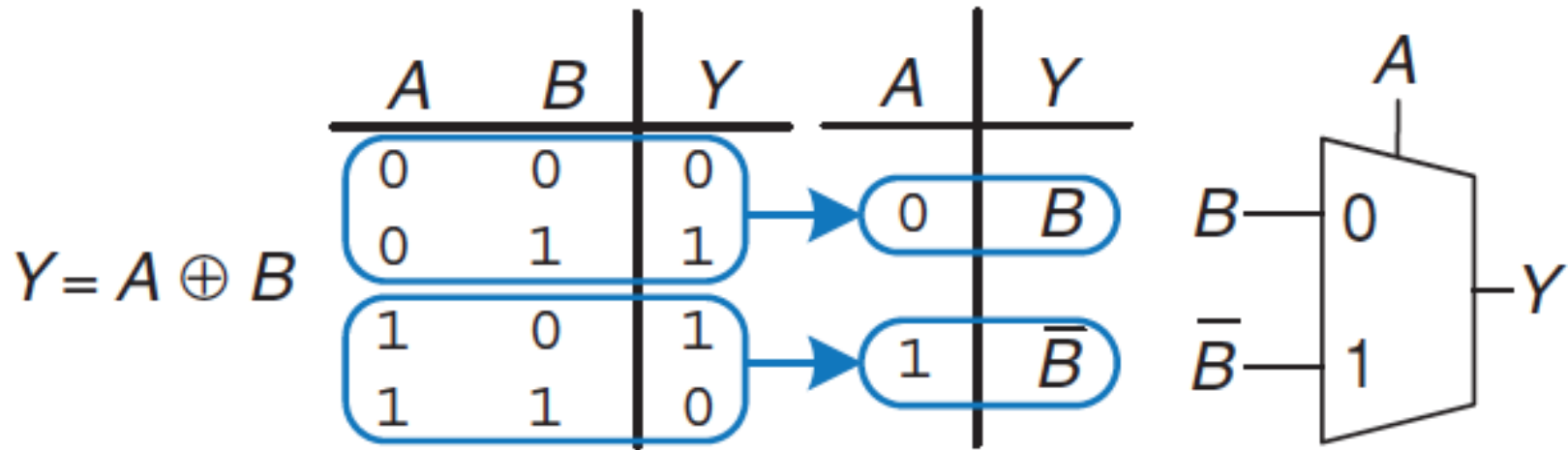- Multiplexers can be used as lookup tables to perform logic functions




Aside: Logic Using Multiplexers (III)

- Multiplexers can be used as lookup tables to perform logic functions

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
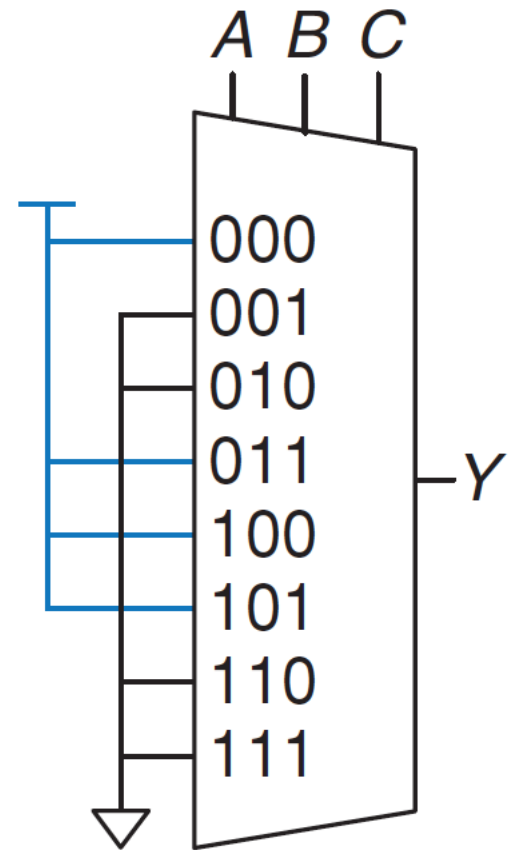
$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$



Aside: Logic Using Decoders (I)

- Decoders can be combined with OR gates to build logic functions.


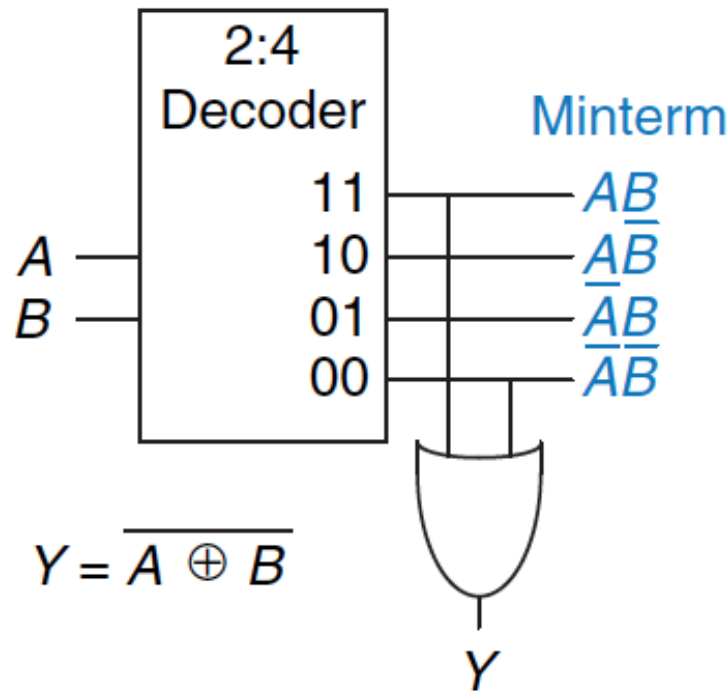


Figure 2.65 Logic function using decoder

Logic Simplification using Boolean Algebra Rules


Recall: Full Adder in SOP Form Logic

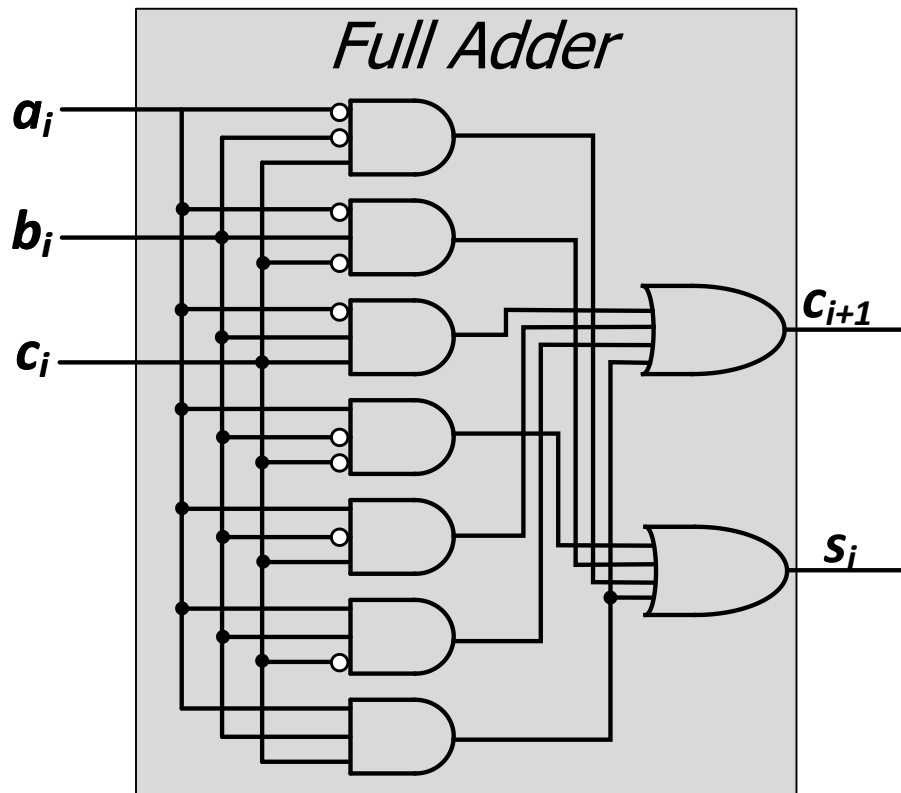

a_i	b_i	$carry_i$	$carry_{i+1}$	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Goal: Simplified Full Adder

Full
Adder

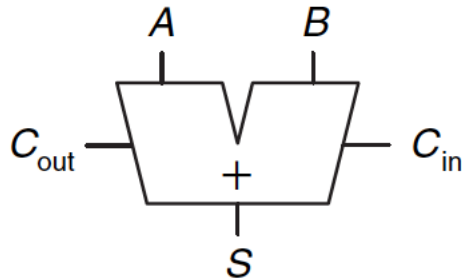

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

How do we simplify Boolean logic?

Quick Recap on Logic Simplification

- The original Boolean expression (i.e., logic circuit) may not be optimal

$$F = \sim A(A + B) + (B + AA)(A + \sim B)$$

- Can we reduce a given Boolean expression to an equivalent expression **with fewer terms**?

$$F = A + B$$

- The **goal** of logic simplification:
 - **Reduce** the number of gates/inputs
 - **Reduce** implementation cost

A basis for what the automated design tools are doing today

Logic Simplification

■ Systematic techniques for simplifications

- amenable to automation

Key Tool: The Uniting Theorem — $F = A\bar{B} + AB$

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1

$$F = A\bar{B} + AB = A(\bar{B} + B) = A(1) = A$$

Essence of Simplification:

Find two element subsets of the ON-set where only one variable changes its value. This single varying variable *can be eliminated!*

value is not needed

→ *B is eliminated, A remains*

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

$$G = \bar{A}\bar{B} + A\bar{B} = (\bar{A} + A)\bar{B} = \bar{B}$$

B's value stays the same within the ON-set rows


A's value changes within the ON-set rows

→ *A is eliminated, B remains*

Logic Simplification Example: Priority Circuit

■ Priority Circuit

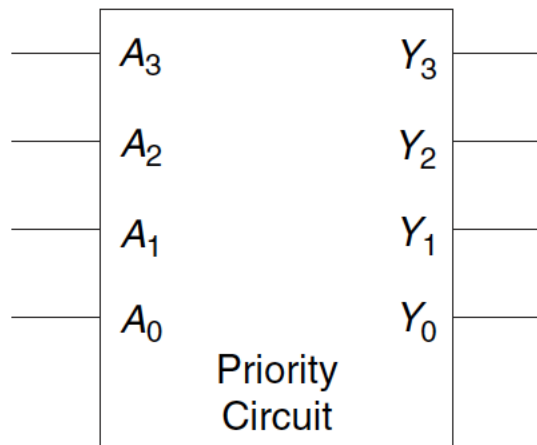- Inputs: "Requestors" with priority levels
- Outputs: "Grant" signal for each requestor
- Example 4-bit priority circuit



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0


Simplified Priority Circuit

- Priority Circuit
 - ❑ Inputs: "Requestors" with priority levels
 - ❑ Outputs: "Grant" signal for each requestor
 - ❑ Example 4-bit priority circuit

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Figure 2.29 Priority circuit truth table with don't cares (X's)

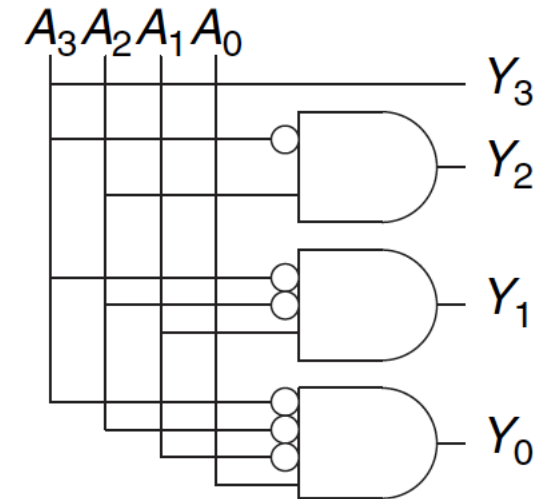

X (Don't Care) means *I don't care what the value of this input is*

Logic Simplification: Karnaugh Maps (K-Maps)

Karnaugh Maps are Fun...

- A pictorial way of minimizing circuits by visualizing opportunities for simplification
- They are for you to **study on your own...**

- See Backup Slides
- Read H&H Section 2.7
- Watch videos of Lectures 5 and 6 from 2019 DDCA course:
 - <https://youtu.be/0ks0PeaOUjE?list=PL5Q2soXY2Zi8J58xLKBNFQFHRO3GrXxA9&t=4570>
 - <https://youtu.be/ozs18ARNG6s?list=PL5Q2soXY2Zi8J58xLKBNFQFHRO3GrXxA9&t=220>

Backup Slides on Karnaugh Maps (K-Maps)

Complex Cases

■ One example

$$C_{out} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

■ Problem

- ❑ Easy to see how to apply Uniting Theorem...
- ❑ Hard to know if you applied it in all the right places...
- ❑ ...especially in a function of many more variables

■ Question

- ❑ Is there an easier way to find potential simplifications?
- ❑ i.e., potential applications of Uniting Theorem...?

■ Answer

- ❑ Need an intrinsically *geometric* representation for Boolean $f()$
- ❑ Something we can draw, see...

Karnaugh Map

- Karnaugh Map (K-map) method
 - K-map is an alternative method of representing the **truth table** that helps **visualize adjacencies** in up to 6 dimensions
 - Physical adjacency \leftrightarrow Logical adjacency

2-variable K-map

$A \backslash B$	0	1
0	00	01
1	10	11

3-variable K-map

$A \backslash BC$	00	01	11	10
0	000	001	011	010
1	100	101	111	110


4-variable K-map

$AB \backslash CD$	00	01	11	10
00	0000	0001	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010

Numbering Scheme: 00, 01, 11, 10 is called a “Gray Code” — only a *single bit (variable) changes* from one code word and the next code word

Karnaugh Map Methods

<i>A</i> \ <i>BC</i>	00	01	11	10
0	000	001	011	010
1	100	101	111	110

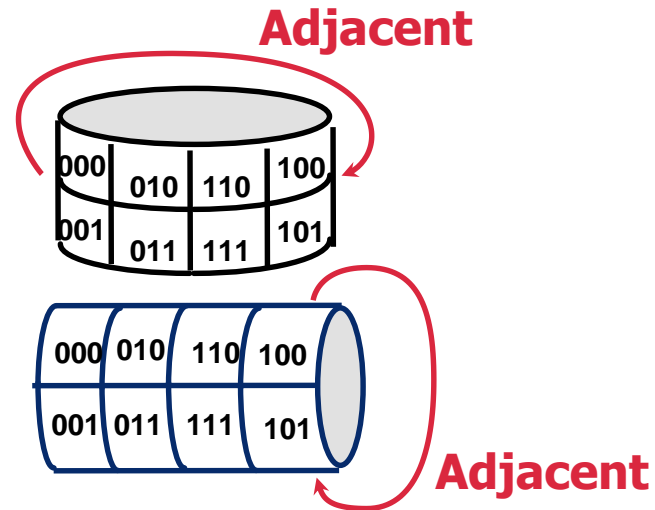

K-map adjacencies go “around the edges”
Wrap around from first to last column
Wrap around from top row to bottom row

K-map Cover - 4 Input Variables

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

$$F(A, B, C, D) = \sum m(0, 2, 5, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$F = A + \bar{B}\bar{D} + B\bar{C}D$$

Strategy for “circling” rectangles on Kmap:

Biggest “oops!” that people forget:

Logic Minimization Using K-Maps


- Very simple guideline:
 - Circle all the rectangular blocks of 1's in the map, using the fewest possible number of circles
 - Each circle should be as large as possible
 - Read off the implicants that were circled

- More formally:
 - A Boolean equation is minimized when it is written as a sum of the fewest number of prime implicants
 - Each circle on the K-map represents an implicant
 - The largest possible circles are prime implicants

K-map Rules

- **What can be legally combined (circled) in the K-map?**
 - Rectangular groups of size 2^k for any integer k
 - Each cell has the same value (1, for now)
 - All values must be adjacent
 - Wrap-around edge is okay
- **How does a group become a term in an expression?**
 - Determine which literals are constant, and which vary across group
 - Eliminate varying literals, then AND the constant literals
 - constant 1 → use X , constant 0 → use \bar{X}
- **What is a good solution?**
 - Biggest groupings → eliminate more variables (literals) in each term
 - Fewest groupings → fewer terms (gates) all together
 - OR together all AND terms you create from individual groups

K-map Example: Two-bit Comparator

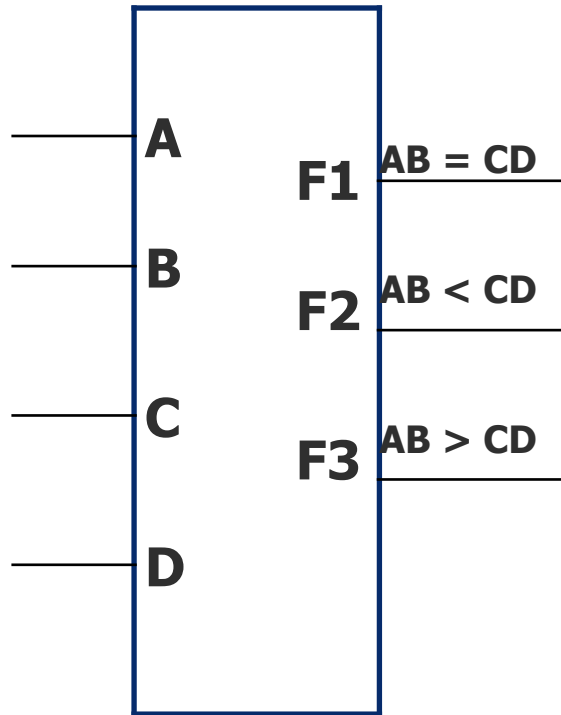


Design Approach:

**Write a 4-Variable K-map
for each of the 3
output functions**

A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

K-map Example: Two-bit Comparator (2)

K-map for F1

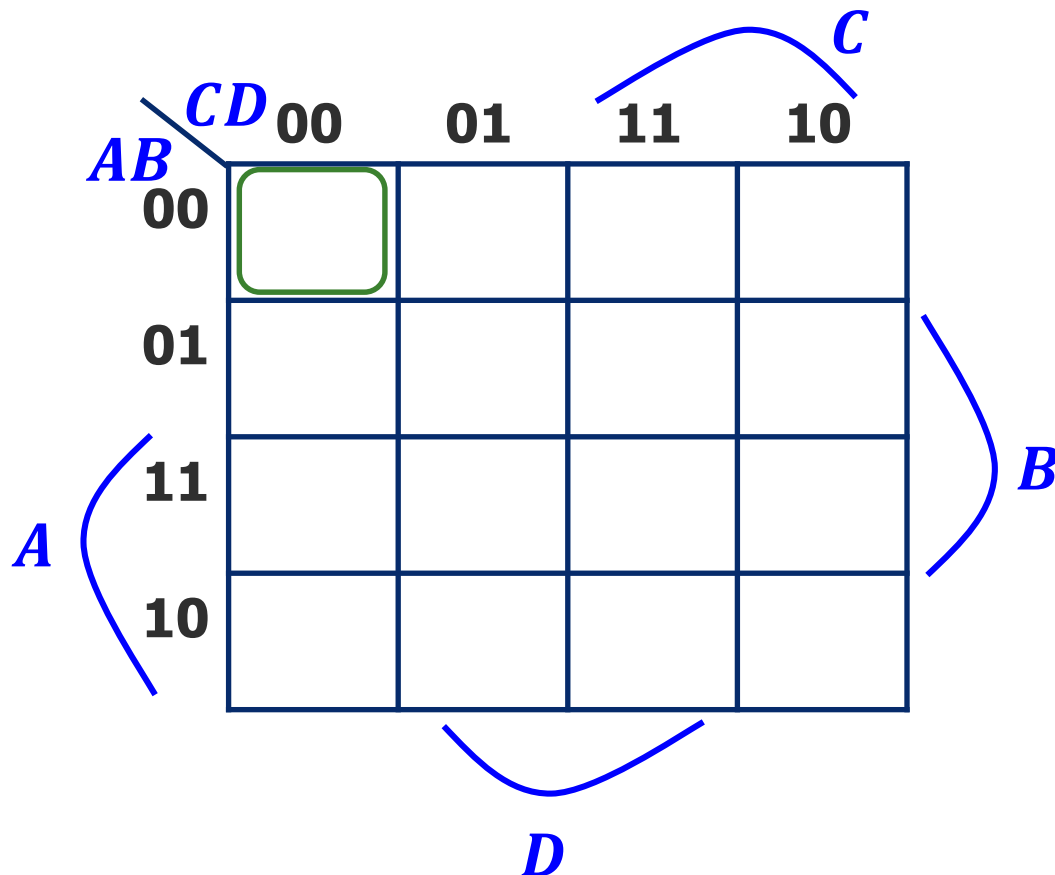


F1 =

A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

K-map Example: Two-bit Comparator (3)

K-map for F2

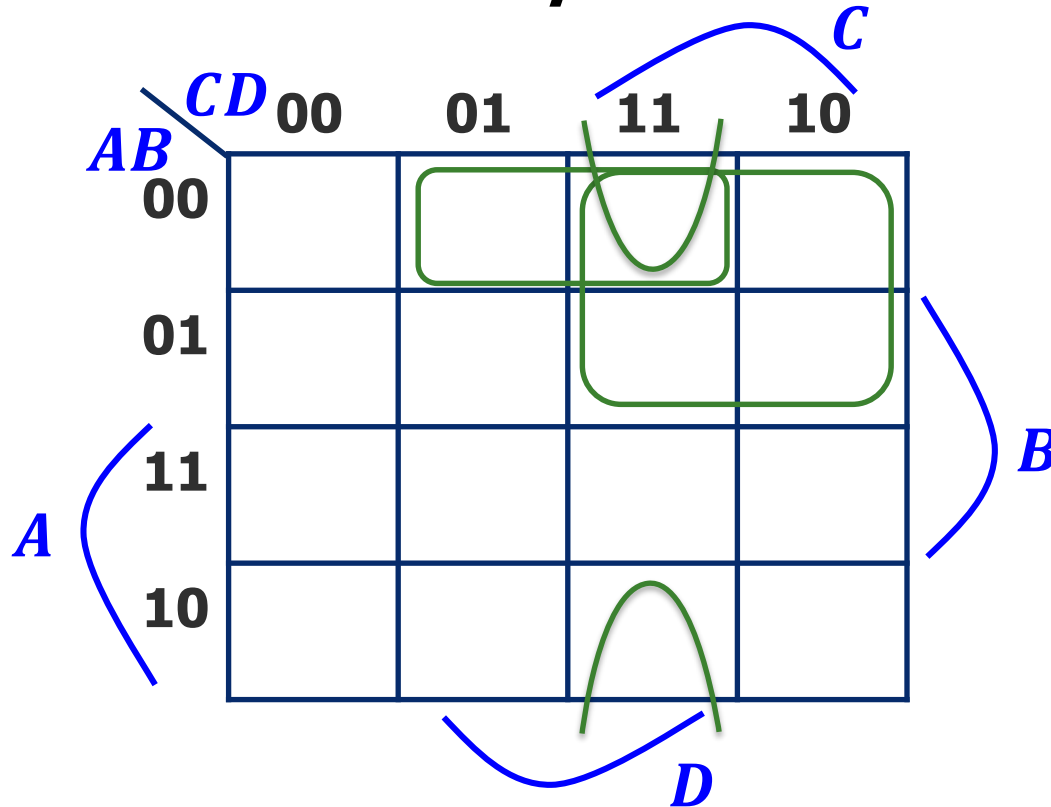

F2 =

F3 = ? (Exercise for you)

A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

K-maps with “Don’t Care”

- **Don’t Care** really means *I don’t care what my circuit outputs if this appears as input*
 - You have an engineering choice to use DON’T CARE patterns intelligently as 1 or 0 to better **simplify** the circuit

A	B	C	D	F	G
...					
0	1	1	0	X	X
0	1	1	1		
1	0	0	0	X	X
1	0	0	1		
...					

I can pick 00, 01, 10, 11 independently of below

I can pick 00, 01, 10, 11 independently of above

Example: BCD Increment Function

- BCD (Binary Coded Decimal) digits
 - Encode decimal digits 0 - 9 with bit patterns 0000_2 — 1001_2
 - When **incremented**, the decimal sequence is 0, 1, ..., 8, 9, 0, 1

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

These input patterns **should never be encountered** in practice (hey -- it's a BCD number!)
So, associated output values are **"Don't Cares"**

K-map for BCD Increment Function

A B

+

W X

Z (without don't cares) =

Z (with don't cares) =

10	1		X	X
----	---	--	---	---

10			X	X
----	--	--	---	---

Y

		CD			
		00	01	11	10
AB	00		1		1
	01		1		1
	11	X	X	X	X
	10			X	X

Z

		CD			
		00	01	11	10
AB	00	1			1
	01	1			1
	11	X	X	X	X
	10	1		X	X

A *B* *C* *D*

K-map Summary

- Karnaugh maps as a formal systematic approach for logic simplification
- 2-, 3-, 4-variable K-maps
- K-maps with “Don’t Care” outputs
- H&H Section 2.7

Digital Design & Computer Arch.

Lecture 5: Combinational Logic II

Prof. Onur Mutlu

ETH Zürich

Spring 2021

11 March 2021